

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

SPH 1202 – ANALOGUE ELECTRONICS

BSC HONOURS PART II: JUNE 2004

DURATION: 3 HOURS

ANSWER **ALL** QUESTIONS IN SECTION A AND ANY **THREE** QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS.

SECTION A

- 1 (a) Explain physical properties of a p-n junction diode which enables it to act as a rectifier. [4]
- (b) Write the voltage-ampere equation for a p-n junction diode and explain the meaning of each symbol. [4]
- (c) Write down the operative functions of a zener diode and explain these functions graphically. [5]
- (d) What is a MOSFET? Write down an expression for drain resistance and show graphically the $I_D - V_{DS}$ circuit characteristics for n – channels in the depletion mode. [5]
- (e) What is Peak Inverse Voltage (PIV)? Determine the output voltage for the bridge rectifier in Figure 1 below. What minimum PIV rating is required for the silicon diodes? [6]

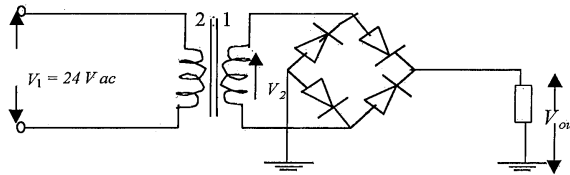


Figure 1

- (f) Determine whether the transistor shown in Figure 2 below is in saturation or not. Assume $V_{CE(sat)}$ is small enough to be neglected. [4]

- (ii) ac load line
Illustrate your answers with the help of a diagram. [4]
- (c) With reference to your answer in (b), explain the term 'Quiescent Point' and its significance on linear and non-linear circuit operations. [4]
- (d) Hence with reference to your answer in Question (c), explain the terms
- (i) cut – off region
- (ii) saturation region
- (iii) linear region [4]
- (e) Provide the defining equation for V_I and V_{out} to highlight some aspects of the circuit operation. Give a brief explanation in each case. [4]
- 4 (a) Give five important characteristics of an operational amplifier and explain virtual ground [7]
- (b) Define common mode rejection ratio and slew rate. If the slew rate is $5 \text{ V}/\mu\text{s}$ at a signal frequency of 0.2 MHz , find the maximum sine wave input voltage. [7]
- (c) Design a circuit using an operational amplifier that will produce an output voltage equal to $-(V_1 + 2V_2 + 0.5V_3)$, where V_1 , V_2 and V_3 are input voltages. [6]
- 5 (a) Draw a block diagram of an oscillator and state the condition necessary for oscillation to take place. [4]
- (b) Draw the circuit diagram of an RC phase shift oscillator and explain its operation. Hence design an RC phase shift oscillator that will oscillate at 100 Hz . [8]
- (d) Draw the circuit diagram of a Wein Bridge oscillator and explain its operation. Hence design a Wein Bridge Oscillator that will oscillate at 25 kHz . [8]
- 6 (a) For a band – pass filter, define
- (i) bandwidth
- (ii) Q – factor
- (iii) Frequency response (sketch) [6]
- (b) On the same diagram, show the Chebyshev; Butterworth and Bessel filter responses. [6]

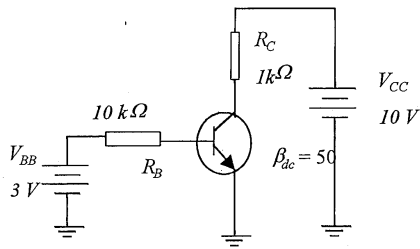


Figure 2

- (g) What is thermal runaway? [4]
- (h) The operational amplifier shown in Figure 3 has an open loop gain equal to 25 000 and an open output resistance of 100Ω . Find
- The magnitude of the loop gain
 - The closed loop gain
 - The input resistance seen by V_{in}
 - The closed loop output resistance
- [8]

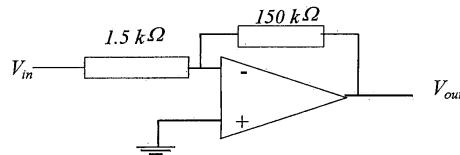


Figure 3

SECTION B

- 2 (a) Determine the ripple factor for the filtered bridge rectifier shown in Figure 4 below. [8]

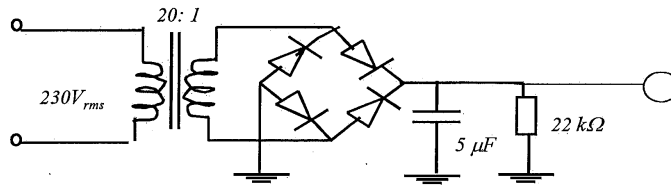


Figure 4

- (b) A 120 Hz full wave rectified voltage with a peak value of 162.6 V is applied to the LC filter in Figure 5 below. Determine the filter output in terms of its dc value and the rms ripple voltage. What is the ripple factor? [8]

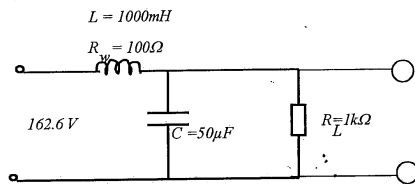


Figure 5

- (c) Comment on the two ripple factors you obtained in (a) and (b). [4]

3 Using Figure 6, below:

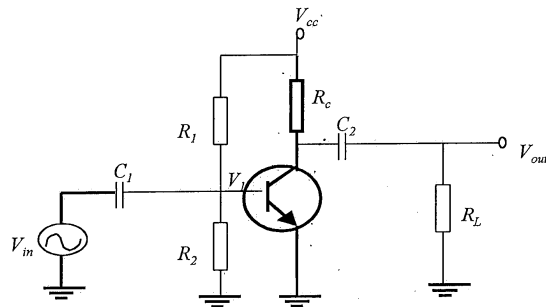


Figure 6

- (a) Explain the functions of C_1 and C_2 . [4]
- (b) Explain the terms
- (i) dc load line

- (c) Design a second order, voltage controlled voltage source (VCVS), low pass Butterworth filter with cut off frequency 2.5 kHz, given the gain in the pass band is 2. [8]

Table 1: Second order low pass filter Butterworth filter design

Circuit element values with resistance in $k\Omega$

| Gain | 1 | 2 |
|-------|----------|------|
| R_1 | 1.32 | 1.20 |
| R_2 | 4.40 | 2.00 |
| R_3 | Open | 5.50 |
| R_4 | 0 | 5.50 |
| C_1 | $0.41 C$ | C |