

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

SPH 1202 – ANALOGUE ELECTRONICS

SUPPLEMENTARY EXAMINATIONS

BSC HONOURS PART II:

AUGUST 2004


DURATION: 3 HOURS

ANSWER **ALL** QUESTIONS IN SECTION A AND ANY **THREE** QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS.

SECTION A

- 1
- (a) Define the following terms
 - (i) doping in semiconductors,
 - (ii) p – type semiconductora and
 - (iii) n – type semiconductor. [6]
 - (b) Derive an equation for the dc-current of full wave rectification. Give reasons for choosing a centre tape rectifier instead of a full wave bridge rectifier [4]
 - (c) Write down the operative functions of a zener diode and explain these functions graphical. [5]
 - (d) What is a MOSFET? Write down an expression for drain resistance and show graphically the $I_D - V_{DS}$ circuit characteristics for n – channels in the depletion mode. [5]
 - (e) What are common-emitter output characteristics for an npn transistor? Illustrate your answer by graphical means. [4]
 - (f) Determine whether the transistor shown in Figure 1 below is in saturation or not. Assume $V_{CE(sat)}$ is small enough to be neglected. [4]

Figure 1

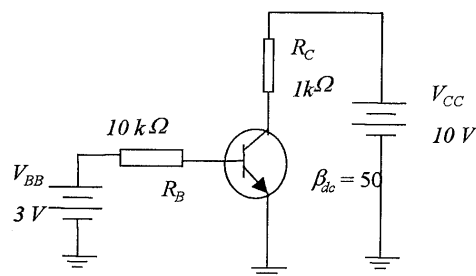

- (g) What is thermal runaway? [4]
- (h) The operational amplifier shown in Figure 2 has an open loop gain equal to 25 000 and an open output resistance of 100Ω . Find
- The magnitude of the loop gain
 - The closed loop gain
 - The input resistance seen by V_{in}
 - The closed loop output resistance
- [8]

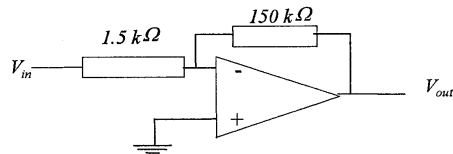


Figure 2

SECTION B

- 2 (a) What is a filter in rectifiers? Write down the differences between a capacitor filter and an inductor filter [10]
- (b) A 120 Hz full wave rectified voltage with a peak value of 162.6 V is applied to the LC filter in Figure 3 below. Determine the filter output in terms of its dc value and the rms ripple voltage. What is the ripple factor? [10]

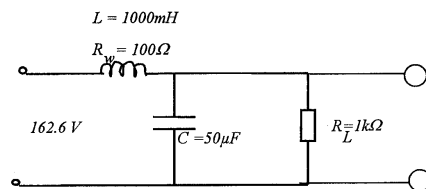


Figure 3

- 5 (a) Draw a block diagram of an oscillator and state the condition necessary for oscillation to take place. [4]
- (b) Draw the circuit diagram of an RC phase shift oscillator and explain its operation. Hence design an RC phase shift oscillator that will oscillate at 100 Hz. [8]
- (c) Draw the circuit diagram of a Wein Bridge oscillator and explain its operation. Hence design a Wein Bridge Oscillator that will oscillate at 25 kHz. [8]
- 6 (a) For a band – pass filter, define
- (i) bandwidth
- (ii) Q – factor
- (iii) Frequency response (sketch) [6]
- (b) On the same diagram, show the Chebyshev, Butterworth and Bessel filter responses. [6]
- (c) Design a second order, voltage controlled voltage source (VCVS), low pass Butterworth filter with cut off frequency 2.5 kHz, given the gain in the pass band is 2. [8]

Table 1: Second order low pass filter Butterworth filter design

Circuit element values with resistance in $k\Omega$

Gain	1	2
R_1	1.32	1.20
R_2	4.40	2.00
R_3	Open	5.50
R_4	0	5.50
C_1	0.41 C	C

END OF EXAMINATION