

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

SPH 1206 – ELECTRICAL CIRCUITS AND ELECTRONICS

BSc HONOURS PART I: MAY 2002


DURATION: 3 HOURS

ANSWER ALL PARTS OF QUESTION 1 IN SECTION A AND ANY 3 QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS

SECTION A


- 1 (a) Describe the use of a transformer as isolation device. [4]
(b) Draw the symbols for NPN and PNP BJTs and N-channel JFET and MOSFET. [4]

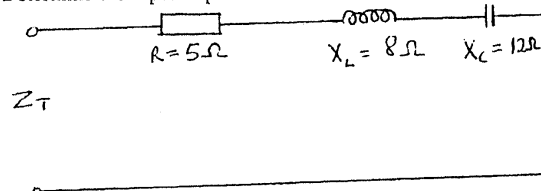(c) Determine the input impedance of the series network



- (d) Compare power diodes and switching diode. Give one application of each. [4]

(e)

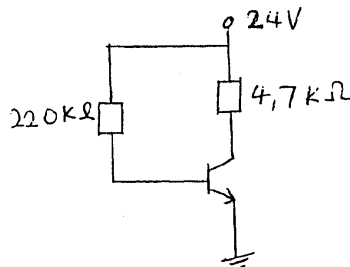

Given that $\beta = 100$, Calculate I_c and V_{CE} [4]

(f) Define the following with respect to semiconductors.

- (a) Leakage current
(b) N - Material


LIBRARY USE ONLY

[4]

(h) Describe drift current in BJTs [4]

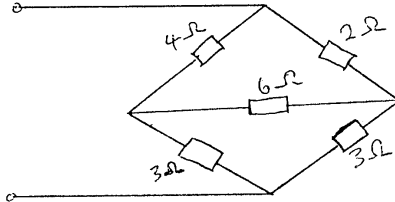
(i) Give the colour coding of the following resistors
37 k Ω , 0,11 k Ω , 98 M Ω , 2,2 k Ω [4]

(j) Find the total resistance of the network.




[4]

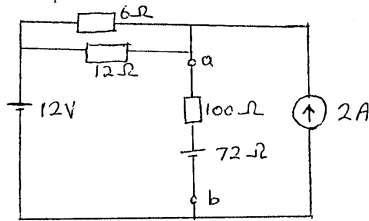2. (a) Find the Norton equivalent circuit for the network external to a - b.



[10]

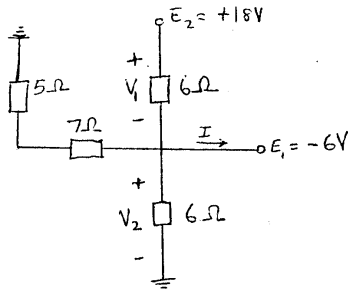
(b) For the network below, determine the voltages V_1 and V_2 and the current I



[10]

begin


(b)

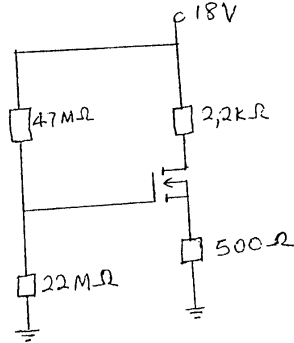

Determine the values of V_{GS} , I_D , and V_{DS} where $V_T = 2V$ $\beta = 0,5 \times 10^3$. [10]

(a) Assuming that the diode on the diagram is biased above the knee and has a bulk resistance of $0,1 \Omega$, find the total current in and total voltage across the diode.

Sketch current versus time.

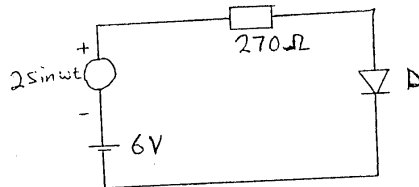

[15]

(b) Give two types of diodes and their applications. [2]


(c) What is a curve tracer [3]

END OF PAPER

LIBRARY USE ONLY

begin


3. *QUESTION 3*

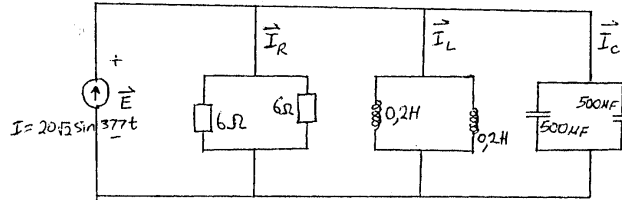

- Compute (a) E , I_R , I_C and I_C
- (b) The total power factor
- (c) Total power delivered to the network
- (d) The impedance of the parallel combination of X_L and X_C [20]

4. (a) A silicon diode has a saturation current of $0,1 \text{ pA}$ at 20°C . Find the current when it is forward biased by $0,6 \text{ V}$. Find the current in the same diode when the temperature is raised to 100°C . Comment on the values of the currents. [10]
- (b) A bar of intrinsic silicon having cross-sectional area of $3 \times 10^{-4} \text{ m}^2$ has an electron density of $1,5 \times 10^{16} \text{ electrons/m}^3$. If $\mu_n = 0,14 \text{ m}^2/(\text{V}\cdot\text{s})$ and $\mu_p = 0,05 \text{ m}^2/(\text{V}\cdot\text{s})$ how long should the bar be in order that the current in it be $1,2 \text{ mA}$ when 9 V is applied across its ends. [10]

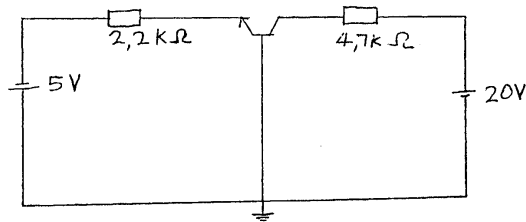5. (a) Determine the equation for the load line of the diagram below. Sketch the load line.



7. a)

A magnetic circuit is made up of steel laminations shaped as shown in *Fig. 6*. The width of the iron is 40 mm and the core is built up to a depth of 50 mm, of which 10 percent is taken up by insulation between the laminations. The air-gap is 2 mm long and the effective

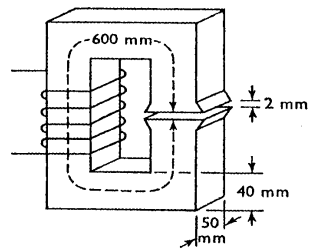


Fig. 6

area of the air-gap is 2500 mm^2 . The coil is wound with 1000 turns. If the leakage factor is 1.2, calculate the magnetising current required to produce a flux of 0.0025 Wb across the air-gap. [20]

LIBRARY USE ONLY

END OF EXAMINATION

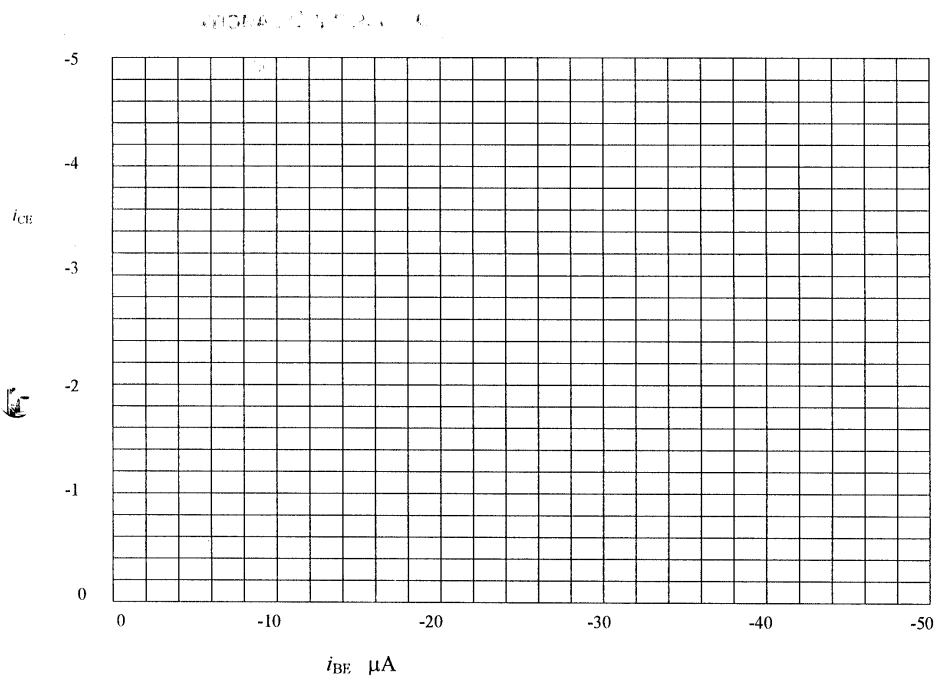


Figure 5d.

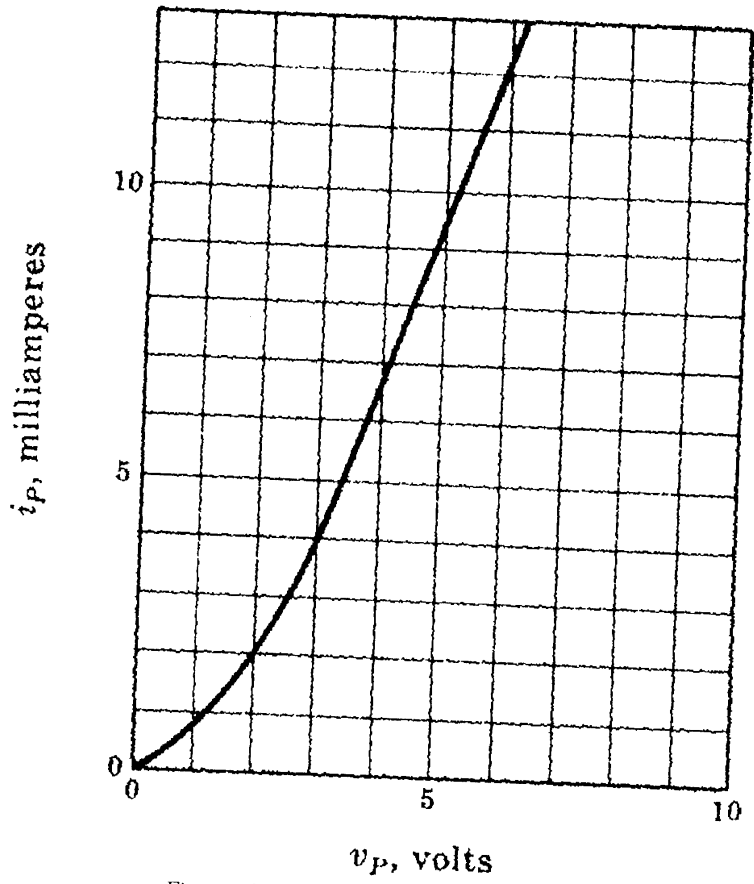


Figure 3b. Diode characteristic curve for diode in Fig. 3a.


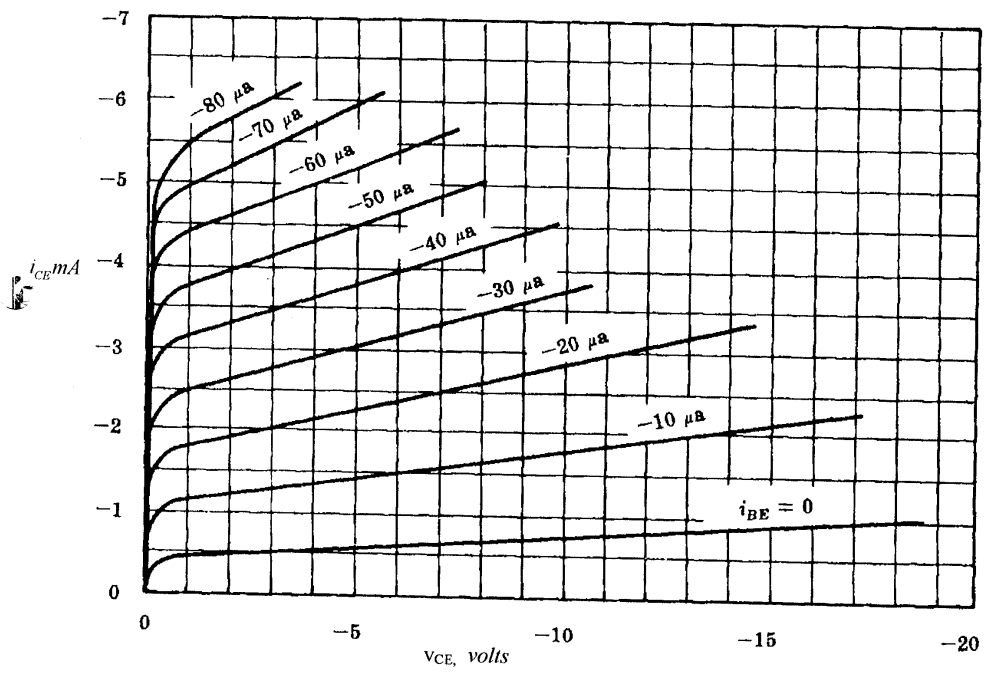


Figure 5b. Transistor static collector characteristics

574 1206

FORMULAE FOR PERFORMANCE FACTORS

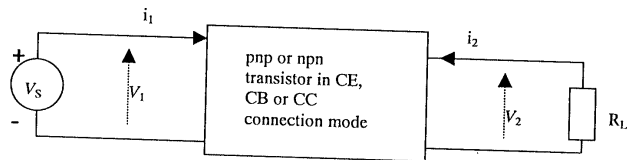

| Performance factor | Formulae |
|------------------------------|--|
| Current Amplification factor | $A_i = \frac{i_2}{i_1} = \frac{h_f}{1 + h_o R_L}$ |
| Input resistance | $R_{in} = \frac{V_1}{i_1} = h_i - h_r R_L A_i = h_i - \frac{h_r R_L h_f}{1 + h_o R_L}$ |
| Voltage amplification factor | $A_v = \frac{V_2}{V_1} = \frac{-A_i R_L}{R_{in}} = \frac{-h_f R_L}{h_i + R_L (h_i h_o - h_r h_f)}$ |
| Power gain | $A_p = A_v A_i = \frac{h_f^2 R_L}{(1 + h_o R_L) [h_i + R_L (h_i h_o - h_r h_f)]}$ |
| Output resistance | $R_{out} = \frac{V_2}{i_2} = \frac{h_i + R_S}{h_o R_S + h_i h_o - h_r h_f}$ |

(V)