

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

SPH 1206 – ELECTRICAL CIRCUITS AND ELECTRONICS

BSc HONOURS PART I: JANUARY 2003

DURATION: 3 HOURS

ANSWER ALL PARTS OF QUESTION 1-IN SECTION A AND ANY THREE QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B 60 MARKS


SECTION A

1. (a) Find the effective values of the following waveforms:

(i) $v = 20 \sin(754t + 30^\circ)$,

(ii) $i = 1.76 \cos(377t - 10^\circ)$. [5]

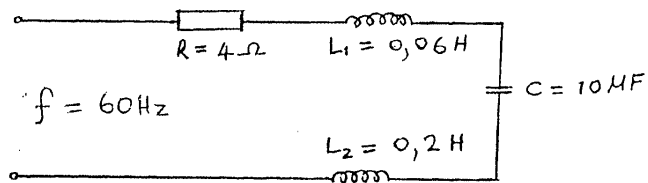- (b) Calculate the impedance of the following circuit. Express your answer in both rectangular and polar form. [6]



- (c) Describe two functions of a transformer. [4]

- (d) In context to a semiconductor, define each of the following terms:


(i) depletion region, [1]

(ii) doping, [1]

(iii) forward bias, [1]

(iv) mobility. [1]

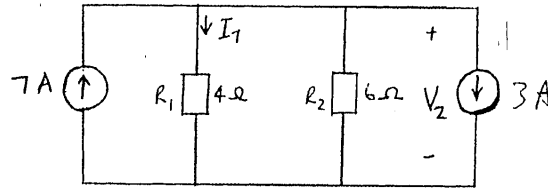- (e) Find the voltage V_2 and current I_1 for the network in the figure below.




[6]

- (f) Give the colour coding of the following resistors:

- (i) $37k\Omega$,
- (ii) 0.11Ω ,
- (iii) $98M\Omega$,
- (iv) $2.2k\Omega$.

[4]


- (g)

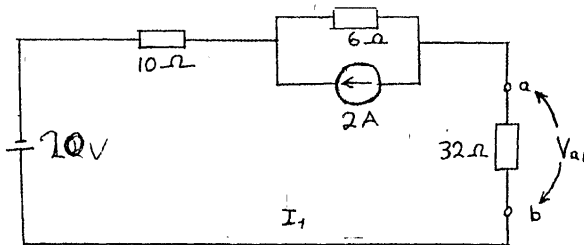

- In the network given above convert the current source and the 6Ω resistor to a voltage source. Find I_1 , V_{ab} and the polarity of points 'a' and 'b'.

[6]

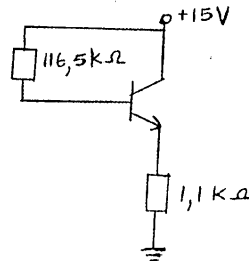
- (h) Find I_B , I_E and V_{CE} for the germanium transistor in the following circuit. Assume $\beta = 120$.




[5]

SECTION B

2.

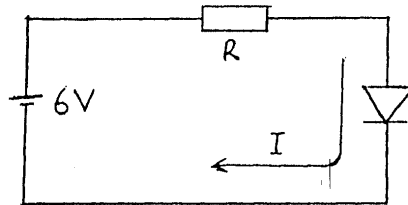


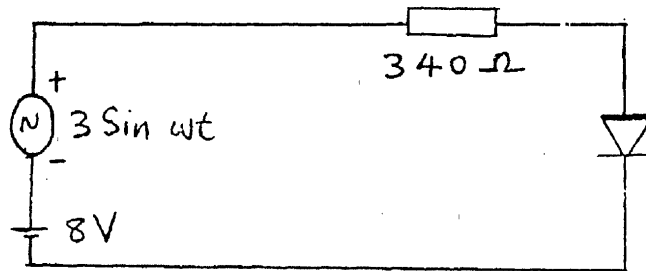- (a) Assuming that the Si diode requires a minimum current of 1mA to be above the knee of its $I - V$ characteristic,
- (i) Calculate the value of R to establish 5mA in the circuit. [3]
 - (ii) For the value of R calculated in (i), find the minimum value to which the voltage E could be reduced and which still maintain the diode above the knee? [5]
- (b) Assuming that the Silicon diode in the circuit below is biased above the knee and has a bulk resistance of 2.0Ω ; find the total current in and total voltage across the diode.



[12]


3.

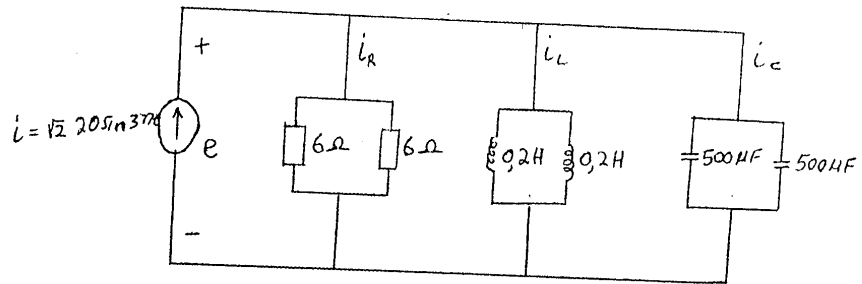

- (a) Compute e , i_R , i_L , and i_C in phasor form.
 (b) Compute the total power factor.

[16]
[4]


4. (a)

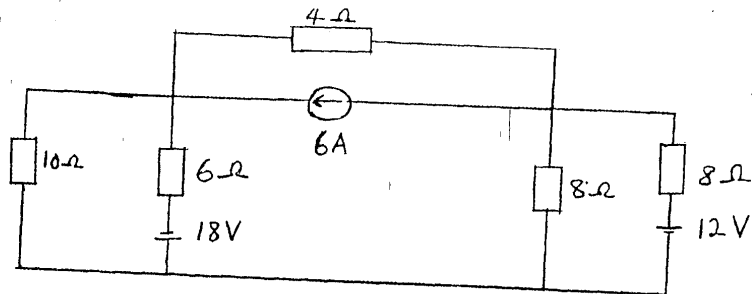


Using Superposition Theorem, find the current through the 10Ω resistor. [20]

5. (a) Determine the equation of load line for the circuit shown below.
 (b) Sketch the line.

[20]

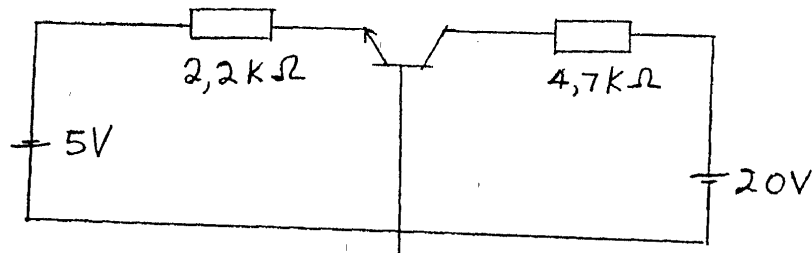


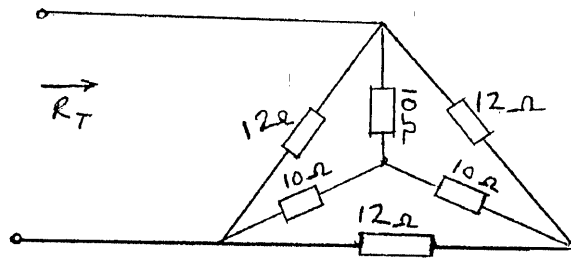6. (a) Find the total resistance of the network in the figure below.



[10]

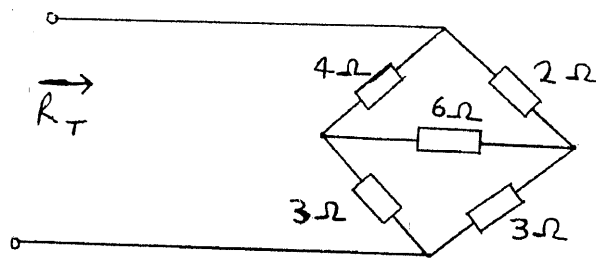- (b) Find the total resistance of the network in the figure below.



[10]

- END OF EXAMINATION PAPER -