

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

SPH 2106 Digital Electronics

SUPPLEMENTARY EXAMINATION

BSC HONOURS PART II : JULY 2003

DURATION : 3 HOURS


ANSWER ALL QUESTIONS IN SECTION A AND ANY THREE QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS.

Planck's Constant	$h = 6.63 \times 10^{-34} \text{ Js}$
Boltzmann's Constant	$k = 1.38 \times 10^{-23} \text{ JK}^{-1}$
Speed of light	$c = 3.00 \times 10^8 \text{ ms}^{-1}$
Charge on an electron	$e = 1.60 \times 10^{-19} \text{ C}$
Mass of an electron	$m_e = 9.10 \times 10^{-31} \text{ kg}$
Permittivity of free space	$\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$
Permeability of free space	$\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$

SECTION A

1. (a) Convert the following numbers into binary numbers:  
(i)  $3258_{10}$ , (ii)  $7543_8$  (iii)  $575.37510$  and (iv)  $175.275_8$  [4]
- (b) Find the value of the following binary operations:  
(i)  $110111 \div 1011$ , (ii)  $11101 * 1110$  (iii)  $11110 + 11011 + 11101$   
and  
(iv)  $10111 - 1011$  [4]
- (c) Write the following numbers in 8421 and 2421 coding systems:  
(i)  $1475_{10}$  and (ii)  $555_8$  [4]
- (d) Use K-map to simplify the following Boolean expressions:  
(i)  $F(ABC) = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$   
(ii)  $X = \overline{A}(BC + B\overline{C}) + A(BC + B\overline{C})$  [8]

 - (e) State and prove De Morgan's theorem. Use the theorem to minimize following functions:
- (i)  $(A+B)(\bar{A}+C)(B+C)=(A+B)(\bar{A}+C)$
- (ii)  $A+BC=(A+C)(A+B)$
- (f) Draw the diagrams for the four input multiplexers and four output demultiplexers. Give one application of each of them. [8]
- (g) Explain the terms: (i) Logic threshold, (ii) Noise Margin and (iii) Propagation Delay. [6]
- (h) How will you realize the following logic using DTL? Give truth table for its operation. [4]



[2]

### SECTION B



2. (a) Show that the "NAND" and "NOR" gates are universal gates. [7]
- (b) A gate is required to monitor two lines, to detect the occurrence of "LOW" level voltages on either or both lines, and to generate a "HIGH" level output used to illuminate an indicator lamp. Draw the circuit and explain the operation. [7]
- (c) A certain gate draws a current of 2 mA when its output is "HIGH" and 3.5 mA when its output is "LOW". What is the average power dissipation if  $V_{CC}$  is 5V and is operated on 50 % duty cycle? [6]
3. (a) What is the difference between half-adder and full-adder? [4]
- (b) Determine the method for implementing full-adder. [8]
- (c) Describe the methods of speeding addition. [8]
4. (a) Draw a diagram for the four stage Johnson Counter. Give the truth table and explain the operation of the counter. [8]
- (b) Draw a ten stage ring counter and show table of its sequence. [8]

(c) If the ten stage ring counter has the initial stage 1010000000, determine the waveform of the Q outputs. [5]

5. (a) Give the performance characteristics of D/A Converter. [7]

(b) Draw the circuit diagram of a "Four Bit Binary Weighted input D/A converter. Explain its operation. [4]

  (c) Determine the output of the D/A converter shown below for the sequence of four bit numbers that are applied to the inputs.  $D_0$  is the LSB. [8]



6. (a) Draw a neat diagram of a "Dual Slope A/D converter and explain its operation. [10]

(b) Explain the terms:

(i) Resolution, (ii) Sampling Rate and (iii) UART

[6]

(c) Determine the resolution for each of the following D /A converters.

(i) Four bit, (ii) six bit and (iii) 18 bit.

[4]

**END OF PAPER**