

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

SPH 2106 – DIGITAL ELECTRONICS

BSc HONOURS PART II: JANUARY 2004
(RADIOGRAPHY)

DURATION: 3 HOURS

ANSWER ALL PARTS OF QUESTION 1 IN SECTION A AND ANY THREE QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS WHILE SECTION B CARRIES 60 MARKS. DRAW NEAT DIAGRAMS WHEREVER NECESSARY.

Speed of light	$c = 3.00 \times 10^8 \text{ ms}^{-1}$
Charge on an electron	$e = 1.60 \times 10^{-19} \text{ C}$
Permittivity of free space	$\epsilon_0 = 8.85 \times 10^{-12} \text{ Fm}^{-1}$
Permeability of free space	$\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$

SECTION A

1. (a) Determine 2's complement of each of the following binary numbers
(i) 1101_2 , (ii) 11100_2 , (iii) 10011_2 and (iv) 10110111_2 [4]
- (b) Perform the following operation using BCD addition.
(i) $00100101 + 00100111$ (ii) $01010001 + 01011000$
(iii) $11110 + 11011 + 11101$ and (iv) $10111 + 1011$ [4]
- (c) Decode the following ASCII coded message.
 $10000011010011100100010011111001011$. [4]
- (d) Write the name *JESUS* in ASCII and EBCDIC code. [6]

(e) Use K-map to simplify the following Boolean expressions:

(i) $F(ABC) = \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC$

(ii) $F(A, B, C, D) = \sum m(4, 5, 7, 12, 14, 15) + \sum d(3, 8, 10)$

[8]

(f) State and prove De Morgan's theorem. Use the theorem to simplify the following functions:

(i) $\overline{\overline{A}B} \cdot \overline{\overline{A}B}B$

(ii) $\overline{A \cdot B} + \overline{A + B}$

[8]

(g) How will you realize the following logic using DTL? Give truth table and explain its operation.



[6]



SECTION B

2. (a) Show that the "NAND" and "NOR" gates are universal gates. [7]

(b) A circuit is required to monitor an automobile safety belt system. An audio signal should be produced to warn a driver that a seat belt is not engaged, when the ignition switch is "ON". The alarm should last for specified time and then turn "off" automatically. Draw a circuit diagram for this system. Give the truth table. [7]

(c) A certain gate draws a current of 2 mA when its output is "HIGH" and 3.5 mA when its output is "LOW". What is the average power dissipation if V_{CC} is 5V and is operated on 50 % duty cycle? [6]

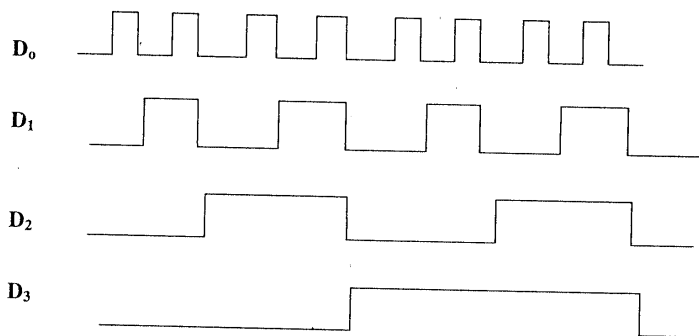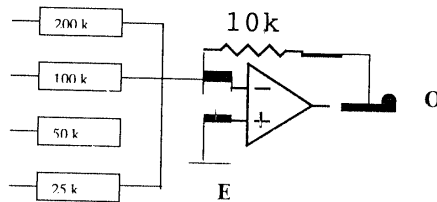3. (a) What is the difference between half-adder and full adder [4]
- (b) Design a "Half Adder" using minimum number of "Nand" gates only. [8]
- (c) Describe the methods of speeding addition. [8]
4. (a) Draw a state and timing diagrams for a BCD decade counter. Explain the operation of a *synchronous* BCD decade counter. [10]
- (b) Draw a ten stage ring counter and show the table of its sequence. [5]
- (c) If the ten stage ring counter has the initial stage 1010000000, determine the waveform of the Q outputs. [5]
5. (a) Give the performance characteristics of a D/A Converter. [4]
- (b) Draw the circuit diagram of a "Four Bit Binary Weighted input D/A converter. Explain its operation. [8]
- (c) Determine the output of the D/A converter shown below for the sequence of four bit numbers that are applied to the inputs. D_0 is the LSB. [8]



6. (a) Draw a neat diagram of a “*successive approximation*” A/D converter and explain its operation. [10]
- (b) Explain the terms:
(i) Resolution, (ii) Sampling Rate and (iii) UART [6]
- (c) Determine the resolution for each of the following D /A converters.
(i) Four bit, (ii) six bit and (iii) 18 bit. [4]

END OF PAPER