

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

SPH 2203: INSTRUMENTATION PHYSICS

BSc HONOURS PART II: MAY 2002


DURATION: 3 HOURS

ANSWER ALL PARTS OF QUESTION I IN SECTION A AND ANY THREE QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS.

SECTION A

1. (a) (i) Define the term uncertainty. [2]
- (ii) A resistance arrangement of 50 ohms is desired. Two resistances of 100.0 ± 0.1 ohms and two resistances of 25.0 ± 0.02 ohms are available. Which should be used, a series arrangement with the 25-ohm resistors or a parallel arrangement with the 100-ohm resistors? Calculate the uncertainty for each arrangement. [4]
- (b) (i) Define the term resolution. [3]
- (ii) If you are using a 10 bit ADC, and wish to read a signal whose range is 2.5 volts, what value of resolution should you expect? [3]
- (c) Four temperature sensors have the following input/output characteristics where $T(t)$ is the temperature as a function of time. Which one is linear?
- (i) $V(t) = aT(t) + b$
- (ii) $V(t) = aT(t - z)$, where z is a constant
- (iii) $V(t) = a \frac{dT(t)}{dt}$
- (iv) $V(t) = e^{aT(t)}$ [4]
- (d) Explain what is meant by 'the order of a system'. [4]

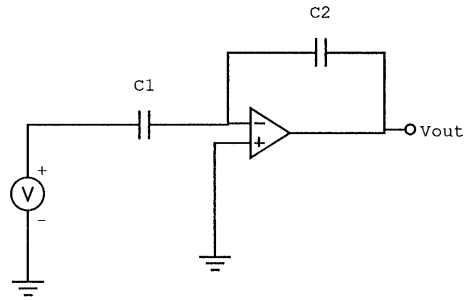- (e) A piezoelectric pressure sensor has an input/output relationship $V = gP_m$ where V = voltage and P_m = pressure. The diagram below is used for signal conditioning for a piezoelectric sensor. Find the transfer function.



[4]

- (f) State four classes of systematic error and give one example of each. [4]
- (g) Using well labelled functional diagrams, show how the following instrumentation blocks can be implemented:
- (i) voltage-to-frequency converter and [4]
- (ii) instrumentation amplifier. [4]
- (h) Differentiate between laminar and turbulent flow in a pipe. [4]

SECTION B

2. (a) We are using a thermistor and a PN junction diode in the opamp circuit to measure temperature. The resistance of the thermistor as well as the current-voltage relationship of the PN junction diode are given as follows:


$$R(T) = R_0 e^{\frac{B}{T - T_0}} \quad \text{and} \quad I = A e^{\frac{qV - E_g}{kT}}$$

LIBRARY USE ONLY


- (i) Draw a schematic diagram for the circuit described. [5]

- (ii) Find the expression for the output voltage of the circuit in terms of the temperature of the thermistor. When the PN junction diode remains at a fixed temperature of T_0 , at all times. [10]
- (b) List five advantages and disadvantages of thermistors over other resistance type thermometers [5]
3. (a) Assume that the output voltage of a sensor is given as:
- $$V_1(T) = \frac{c_1}{T} + c_2$$
- , which is a non-linear relationship.
- In the narrow region of interest, $T_1 - T_2$, it is derived to use the relationship $V_2(t) = K_1T + K_2$ to approximate the above non-linear relationship. Show the steps to be followed to find the maximum error from this approximation. [10]
- (b) Define the Johnson noise density for a resistive element. [3]
- (c) If a resistive sensor is connected in a voltage divider circuit, discuss the effect of both the Johnson noise and the supply voltage on the performance of the sensor system. [7]
4. (a) For a system of two semi-circular plates in which the overlapping area alters with angular displacement of a common shaft,
- (i) derive the transfer function of the system for any dielectric, [5]
- (ii) what is the responsivity of the system and [3]
- (iii) suggest one method that can be used to increase the responsivity. [2]
- (b) Using diagram where applicable, discuss the following:
- (i) auto – correlation, and
- (ii) dual sensitivity in load cells. [10]

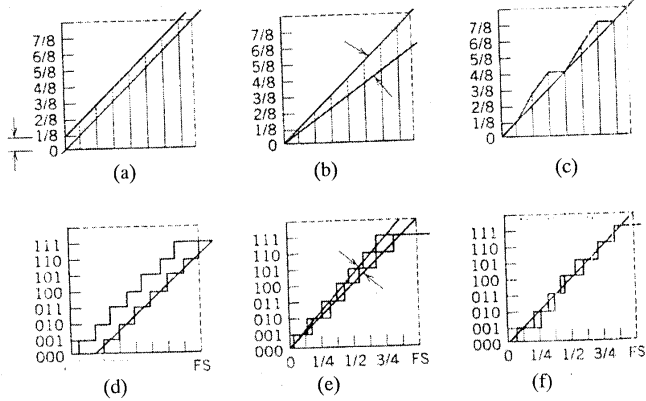4. (a) Name the ADC and DAC errors depicted in the calibration curves (a) – (f). Specify which ones are ADC or DAC errors. [6]



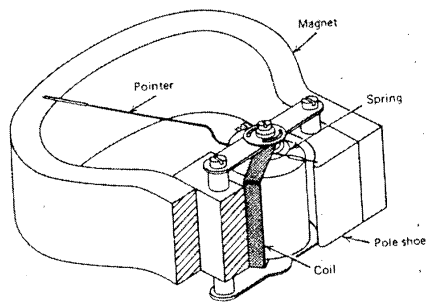- (b) Name the instrument below. With the use of appropriate equations, describe how this instrument works. [10]



- (c) Calculate the value of the multiplier resistance on the 50-V range of a dc voltmeter that uses a 500- Ω meter movement with an internal resistance of 1 k Ω . [4]
6. (a) State the assumptions involved in deriving Bernoulli's equation. [3]
- (b) Write down Bernoulli's equation and explain all the terms in the equation. [5]
- (c) Using a well labelled diagram, describe any one of the following:
- (i) Orifice meter, and [6]
- (ii) venturi meter. [5]

- END OF PAPER -