

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

DIGITAL ELECTRONICS SPH 2206

SUPPLEMENTARY EXAMINATION

BSC HONOURS PART II : JULY 2001

DURATION: 3 HOURS

ANSWER **ALL** PARTS OF QUESTIONS 1 IN SECTION A AND ANY **THREE** QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS.

LIBRARY USE ONLY

SECTION A

- Q1. (a) Determine the resolution of a 12 – bit D/A converter in terms of percentage. [3]
- (b) Draw the block diagram of a successive approximation A/D converter. [3]
- (c) Show the use of a Schmitt trigger in interfacing systems with transmission lines. [3]
- (d) Draw a four – bit parallel adder and determine the sum and carry outputs of each adder for the inputs $A = 1001$ and $B = 1010$ [5]
- (e) If the wave forms in fig 1 are applied to an $\bar{S}-\bar{R}$ latch, sketch the resulting Q output waveform in relation to the inputs. Assume Q starts LOW.

 


Fig. 1

- (f) For the logic circuit in Fig. 2, sketch the output waveform in proper relation to the inputs.

 
 


Fig. 2

- (g) The simultaneous occurrence of two HIGH level voltages must be detected and indicated by a LOW level output that is used to illuminate an indicator lamp. Sketch the operation. [5]
- (h) Simplify the circuit of Fig. 3 as much as possible and verify that the simplified circuit is equivalent to the original by showing that their truth tables are identical.

 


Fig. 3

[5]

- (i) For the edge triggered $J-K$ flip-flop with pre-set and clear inputs, determine the Q output for the inputs shown in the timing diagrams of Fig. 5. Q is initially LOW.

 


Fig. 4

[6]

SECTION B

2. (a) A 12-bit D/A converter has an initial accuracy of $\frac{1}{4}$ LSB and a differential non linearity temperature coefficient of $4.0 \text{ ppm}/^\circ\text{C}$. The converter is to be used in an environment that goes from $+25^\circ\text{C} \leq T \leq 75^\circ\text{C}$. Is monotonicity assured. For a 12-bit converter, $1\text{LSB} = 244\text{ppm}$. [10]
- (b) Draw a five-bit register using D-flip-flops. Show the states of the register for the specified data input and clock waveforms shown in Fig. 5. Assume the register is initially cleared (all 0s) [10]

 


Fig. 5

3. (a) Draw the diagram of a synchronous BCD decade counter. Analyse the operation and draw the timing diagram. [10]
- (b) Draw the block diagram of a digital 12 hour clock with six 7 segment readouts. [10]
4. Write brief notes on
- (a) parity generators [5]
- (b) CMOS inverter [5]
- (c) R/2R resistive ladder DAC [5]
- (d) Intergrated injection logic (I^2L) [5]
5. (a) Draw the diagram of a three stage synchronous binary counter and draw its sequence of states table. [10]
- (b) Draw the diagram of a four stage Johnson Counter draw the table of its sequence. [10]
6. (a) Show the J - K flip-flop making transition from RESET to SET state. [10]
- (b) A 555 timer is to be used as an unstable multivibrator. Determine the values of R_1 and R_2 if the output frequency is to be 10kHz with a duty cycle of 50%. The capacitor C is $0.1\ \mu\text{F}$. [10]

END OF PAPER