

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

SPH 2206 DIGITAL ELECTRONICS

BSc HONOURS PART II : MAY 2002

DURATION : 3 HOURS

ANSWER ALL PARTS OF QUESTION 1 SECTION A AND ANY THREE QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS.

SECTION A

- 1 (a) Write brief notes on
- (i) Small-Scale Integration SSI. [6]
 - (ii) Medium-Scale Integration MSI
 - (iii) Logic analyzer. [6]
- (b) Discuss the schmitt trigger as an interface circuit [5]
- (c) (i) Use Karnaugh Map to find the minimum sum-of-products form for the given expression. [3]
- $$X = \bar{A}(BC + B\bar{C}) + A(BC + B\bar{C})$$
- (ii) Simplify, using Boolean algebra: [3]
- $$\bar{A}\bar{B}C + (A + B + \bar{C}) + \bar{A}\bar{B}\bar{C}D$$
- (d) State De Morgan's theorems. Illustrate the use of logic gates to obtain the theorems. [6]
- (e) (i) Convert $B2F8_{16}$ to decimal.
- (ii) Find $DF_{16} + AC_{16}$.
- (iii) Convert from decimal to BCD : 65
- (iv) Convert to excess -3 code : 35 [4]

STAFF USE ONLY

- (f) If the input waveforms are applied to the decoding logic, as indicated in fig 1, sketch the output waveform in proper relation to the inputs. [4]

 


Fig. 1

- (g) Using a 555 timer, design an astable multivibrator that will produce a clock signal at a frequency of 10KHz and 50% duty cycle. Use a $0.1\mu\text{F}$ capacitor. [5]
- (h) For the edge triggered J - K flip - flop with preset and clear inputs, determine the Q output for the inputs shown in the timing diagram of fig 2. Take Q to be initially at a low value. [4]

 


Fig. 2

SECTION B

2. (a) Draw the diagram of a BCD decade counter. Analyse its operation and draw the timing diagrams. [10]
- (b) Show the master - slave J - K flip-flop, making transition from RESET to SET. [10]

3. (a) Draw the circuit for an R – 2R resistive ladder D/A converter. If $R = 10k\Omega$ and $V = 10V$, determine the analogue voltage given that the digital input is 1001. [10]
- (b) Draw a 4 – bit shift register, using J. K. flip-flops. Assume that all the Q outputs are initially clear. The data word to be loaded into the shift register is 0101. Explain how this is achieved. [10]

4. (a) Draw a four-bit parallel adder in the block diagram form. Determine the sum and carry outputs of each adder for the inputs 1011 + 1110. [10]
- (b) (i) Apply De-Morgan theorem to the following expression.

$$\overline{A + B + C + D} + \overline{ABCD} \quad [5]$$

- (ii) Convert the following to sum-of-product form and minimise.

$$AB + CD(A\bar{B} + CD) \quad [5]$$

5. Write brief notes on

- (i) Integrated injection logic (I²L) [5]
 (ii) Parity generators [5]
 (iii) CCD registers [5]
 (iv) UART interface [5]

6. (a) Explain the working of a floppy disk used as a memory device [6]
- (b) Draw a typical PROM block diagram and write brief notes on the PROM. [8]
- (c) Discuss the characteristics of the following: EPROM, UVEEPROM, and EEPROM. [6]

- END OF PAPER -