

**NATIONAL UNIVERSITY OF SCIENCE AND
TECHNOLOGY**

APPLIED PHYSICS DEPARTMENT

SPH 2206 - DIGITAL ELECTRONICS

BSc HONOURS PART II: JUNE 2004

DURATION: 3 HOURS

ANSWER **ALL** PARTS OF SECTION A AND ANY **THREE** IN SECTION B.
SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS


SECTION A

1. (a) Perform the following operations using 1's and 2s-complement method.
(i) $11100 - 1101$, (ii) $100001 - 1010$, (iii) $10111 - 11111$ [6]
- (b) Perform the following operation using *BCD* addition.
- (i) $00100101 + 00100111$
(ii) $01010001 + 01011000$
(iii) $11110 + 11011 + 11101$ and
(iv) $10111 + 1011$ [4]
- (d) Write the name *JESUS* in ASCII and EBCDIC code. [8]
- (e) Use K-map to simplify the following Boolean expressions:
- (i) $F(ABC) = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$
(ii) $F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 8, 10) + \sum d(9, 11, 12, 14)$ [4]
- (f) State and prove De Morgan's theorem. Use the theorem to simplify the following functions:
- (i) $\overline{(\overline{A.B}).A(\overline{A.B})B}$
- (ii) $\overline{A.B} + \overline{\overline{A} + B}$ [4]

- (g) How will you realize the following logic using DTL? Give truth table and explain its operation. [6]



 
- (h) Explain the operation of the circuit given below. Calculate the out put voltage at point O. If the logic 1 threshold is 3.8 V, calculate the minimum value of R_2 to obtain logic 1 at the out put. What is the effect of reducing the value of R_1 ? [8]




SECTION B

2. (a) Show that the "NAND" and "NOR" gates are universal gates. [8]
- (b) A circuit is required to monitor an automobile safety belt system. An audio signal should be produced to warn a driver that seat belt is not engaged, when ignition switch is "ON". Alarm should last for specified time and then turn "off" automatically. Draw a circuit diagram for this system. Give truth table. [7]

 - (c) A certain gate draws a current of 2 mA when its output is "HIGH" and 3.5 mA when its output is "LOW". What is the average power dissipation if V_{CC} is 5V and is operated on 50 % duty cycle? [5]
3. (a) What is the difference between half-adder and full adder [4]
 (b) Design a "Half Adder" using minimum number of "NOR" gates only. [8]
 (c) Describe the methods of speeding addition. [8]
4. (a) What do you understand by *race around condition* in a flip-flop? How this condition can be avoided? [6]
 (b) Draw a state and timing diagrams for a BCD decade counter. Explain the operation of a *synchronous* BCD decade counter. [8]
 (c) If the ten stage ring counter has the initial stage 101000000, determine the waveform of the Q outputs. [6]
5. (a) Give the performance characteristics of D/A Converter. [4]
 (b) Draw the circuit diagram of a "Four Bit Binary Weighted input D/A converter. Explain its operation. [8]
 (c) Determine the output of the D/A converter shown below for the sequence of four bit numbers that are applied to the inputs. D_0 is the LSB. [8]



 

6. (a) Draw a neat diagram of a “*successive approximation*” A/D converter and explain its operation. [10]
- (b) Explain the terms:
- (i) Resolution,
 - (ii) Sampling Rate and
 - (iii) UART [6]
- (c) Determine the resolution for each of the following D /A converters.
- (i) Four bit,
 - (ii) six bit and
 - (iii) 18 bit. [4]

END OF PAPER