

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

APPLIED PHYSICS DEPARTMENT

SPH 2206– DIGITAL ELECTRONICS

BSc HONOURS RADIOGRAPHY: PART II:

APRIL 2014 EXAMINATION

DURATION: 3HOURS

ANSWER **ALL** PARTS OF QUESTION **ONE** IN SECTION **A** AND ANY **THREE** QUESTIONS FROM SECTION **B**. SECTION **A** CARRIES 40 MARKS AND SECTION **B** CARRIES 60 MARKS.

SHOW ALL YOUR STEPS CLEARLY IN ANY CALCULATION.

SECTION A

1. (a) Briefly explain why D type flip flops are most suitable in the design of shift Registers. [2]
- (b) For the pulse shown below in Fig 1, Determine:-
- (i) rise time; [2]
 - (ii) fall time; [2]
 - (iii) pulse width; [2]
 - (iv) amplitude of the waveform [2]

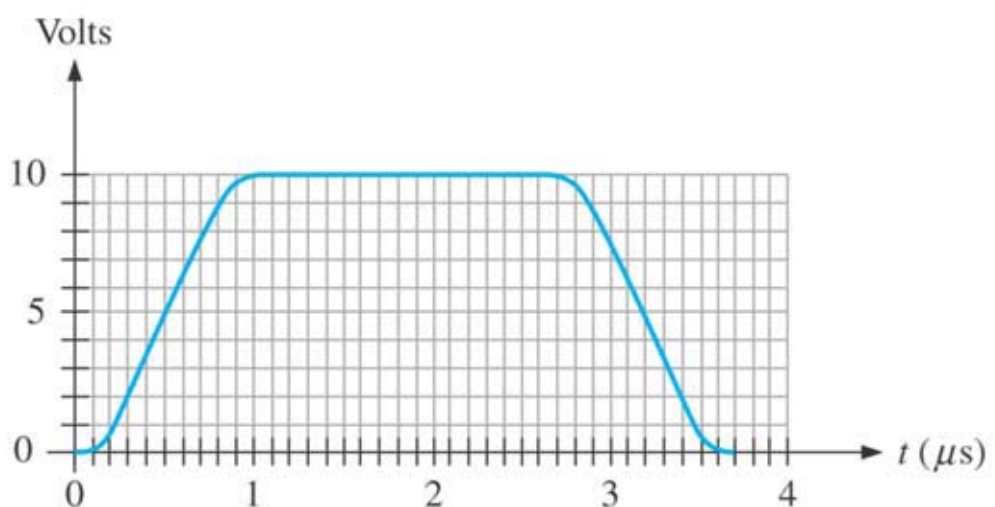


Fig 1: Voltage vs time waveform graph

- (c) Convert the following decimal numbers to binary, octal and hexadecimal.
- (i) 749.026_{10} [3]

(ii) 657.087_{10}

[3]

- (d) Convert the following logic gate circuit in Fig 2, into a Boolean expression, writing Boolean sub-expressions for each gate output in the diagram.

[6]

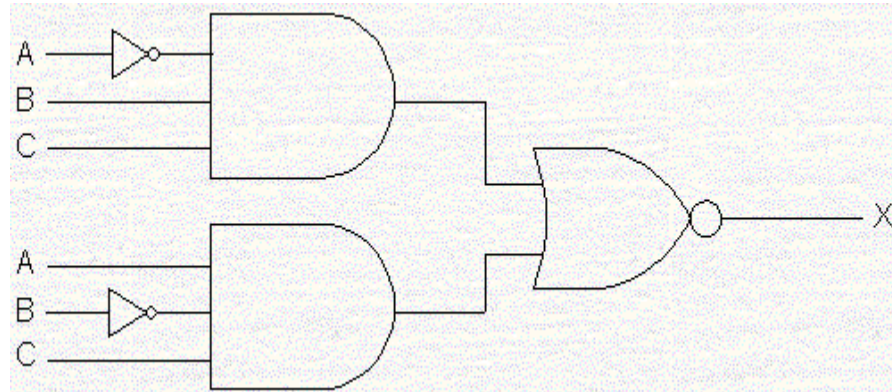


Fig 2: Combinational Logic Circuit

- (e) A Radiography engineer hands you a piece of paper with the following Boolean Expression.

$$\overline{A}B + \overline{C}[A + B]$$

Draw a logic gate circuit for this function.

[4]

- (f) Suppose you needed an inverter gate in a logic circuit, but none were available. You do, however, have spare (unused) NAND gates in one of the integrated circuits.

- (i) Show how you would connect a NAND gate to function as an OR gate. [4]
(ii) Use Boolean algebra to show that your solution is valid. [4]

- (g) Perform the following subtraction using the 2's complement method.

(i) $10101_2 - 10111_2$ [2]

(ii) $1111000_2 - 1111111_2$ [2]

- (h) Compute a truth tables for the Boolean expression

$$\text{Output} = A + \overline{A}B$$
 [2]

SECTION B

2. (a) The control logic for an x - ray heating system is to operate as follows: During the daytime, heating is required only if the temperature falls below 68°C . At night, heating is required only for temperatures below 62°C . Assume that logic signals D, L, and H are available. D is high during the daytime and low at night. H is high only if the temperature is above 68°C . L is high only if the temperature is above 62°C . Design a logic circuit that produces an output signal F that is high only when heating is required. [9]
- (b) Define each of the following:
- (i) Commutative property [1]
 - (ii) Associative property [1]
 - (iii) Distributive property [1]
- (c) Implement the following Boolean functions using simple AND, OR and NOT logic gates. (Do not simplify the functions):
- (i) $F = AB + ABC + CD$ [2]
 - (ii) $F = A BC + ABC + A B$ [2]
 - (iii) $F = X Y Z (W + YZ) + ZW + X Y$ [4]
3. (a) Examine the truth table in Fig 3 below.

A	B	C	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Fig 3: Three input Truth Table

- (i) Write both SOP and POS Boolean expressions describing the Output [4]
(ii) Which of those Boolean expressions is simpler for this particular truth table? [2]
- (ii) Use any technique of your choice to show that the two Boolean expressions are the same. [5]
- (b) (i) What is a shift register. [1]
(ii) Explain the operation of the following registers SISO, SIPO, PISO and PIPO. [8]
4. (a) Define each of the following terms as used in digital electronics
(i) Encoder [2]
(ii) Decoder [2]
(iii) Multiplexer [2]
(iv) De-multiplexer [2]
- (b) Design a multiplexer with four input data lines and a single output line. [8]
- (c) (i) What is meant by the word *resolution* in reference to an ADC or a DAC? [2]
(ii) Why is resolution important to us, and how may it be calculated for any particular circuit knowing the number of binary bits? [2]
5. (a) (i) Design a four-bit binary up counter circuit, using J-K flip-flops. [14]
(ii) Explain what would happen if the upper AND gate's output is to become stuck" in the high state regardless of its input conditions. [2]
(iii) What effect would this kind of failure have on the counter's operation? [2]
- (b) Use De – Morgan's theorems to simplify the following expressions:
- (i) $F = \overline{\overline{\overline{(A+B)}(C+D)}(E+F)(G+H)}$ [1]
- (ii) $F = \overline{[\overline{A+B+C}][\overline{AB\overline{C}D}]}$ [1]
6. (a) (i) Compute a truth table for a full adder . [4]
(ii) Obtain the logic expressions for the sum and carry from the truth table. [4]
(iii) Implement the simplified logic circuit. [2]
- (b) Draw the circuit diagram of a clocked JK flip-flop using NOR gates and explain circuit action for all combinations of input states. [6]
- (c) Simplify the following using K- map
(i) $F = \sum (0, 2, 4, 6, 8, 10, 12, 14)$ [2]
(ii) $F = \sum (0, 1, 2, 3, 5, 7, 8, 9, 10, 11)$ [2]

THE END