

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

FACULTY OF INDUSTRIAL TECHNOLOGY
BACHELOR OF ENGINEERING (HONS) DEGREE

Final Examination May 2013

Analogue Electronics

TEE 1211

Duration of Examination 3 Hours

Instructions to Candidates:

1. Answer any **five** questions only.
2. Each question carries equal marks.
3. Show all your steps clearly in any calculation.
4. Start the answers for each question on a fresh page.

Question 1

For the amplifier shown in diagram Fig 1 the transistor T1 has a β equal to 100
Determine the following bias working parameters:

- (a) Base current I_B ;
 - (b) the collector current I_C
 - (c) the emitter current I_E
 - (d) the voltage across the collector to the ground V_C
 - (e) and the voltage across the collector-emitter V_{CE} .
- (20 marks)

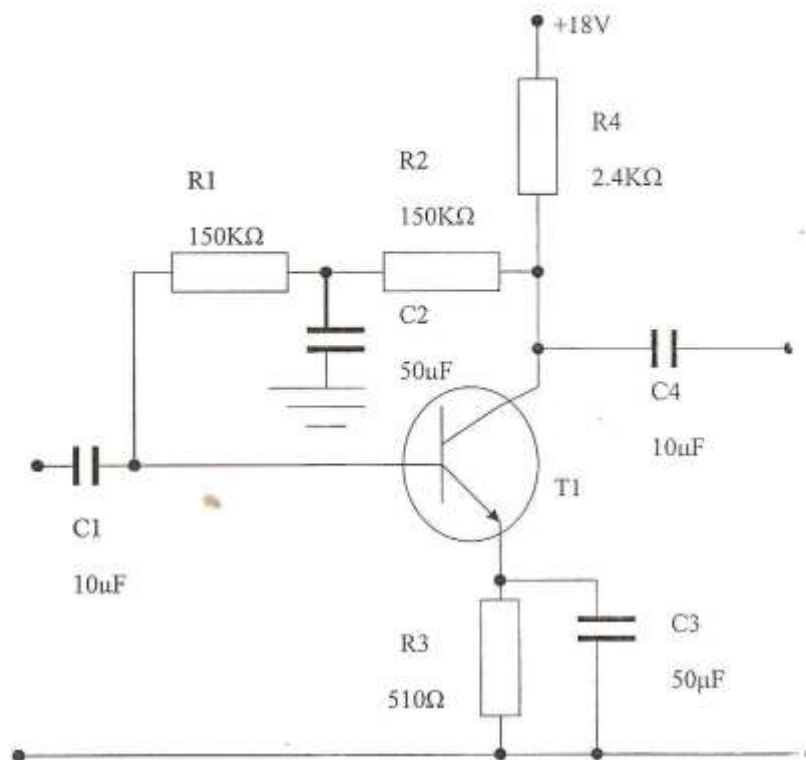


Fig 1

Question 2

- (a) A shunt zener diode regulator has an input unregulated voltage of 20 volts. The zener is a 15 volts one. Calculate a suitable value of the series resistor R_S that can be used for the load current I_L that vary from 20mA to 40mA. Choose the suitable maximum power for the zener diode. Draw the circuit diagram for regulator. (10 marks)
- (b) Draw the circuit of a transistor RC phase shift oscillator. Briefly describe the oscillator in terms of reason of choice components determining the output frequency. (10 marks)

Question 3

- (a) Show the circuit diagram of a tripler. Give one example where this circuit is applied.

(8 marks)

- (b) For the circuit shown in Fig 2, R_{EE} equal $10K\Omega$ h_{fe} for T1 and T2 equal 100. Calculate the values of R1 and R2 that will make the difference gain equal 500. (12 marks)


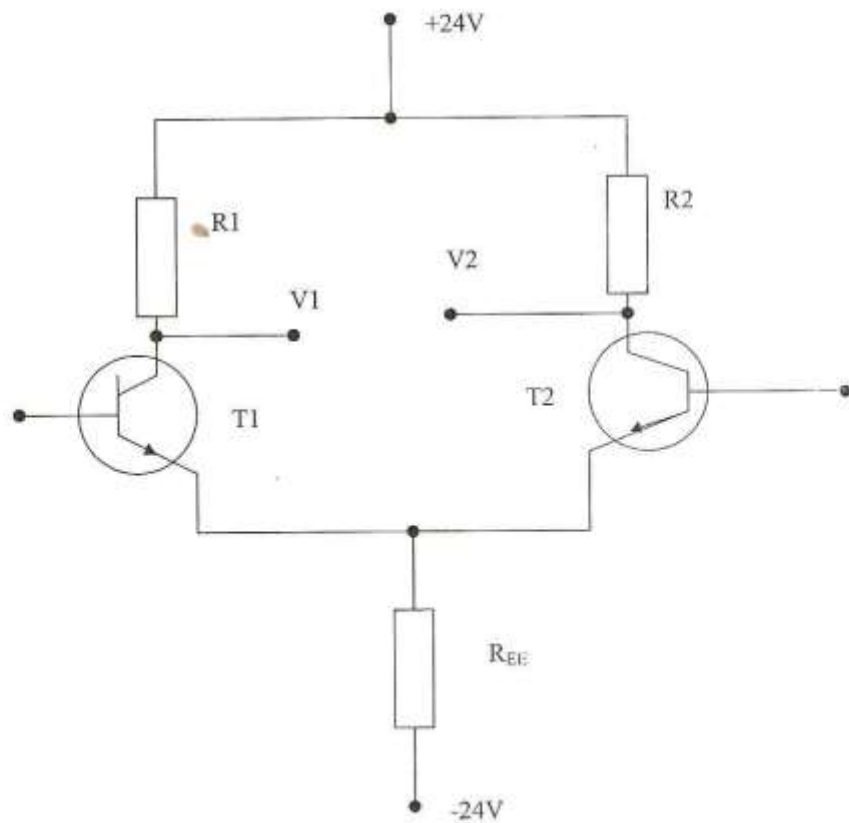
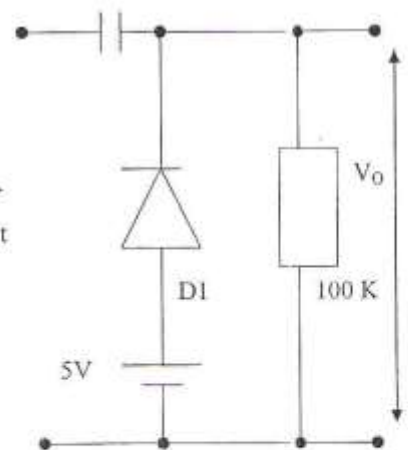


Fig 2

Question 4

- (a) Find the voltage, input impedance, and output impedance for a series negative feedback amplifier having gain of 200, feedback factor of 0.1, input resistance of $100\text{K}\Omega$ and output resistance of $470\text{K}\Omega$. (15 marks)
- (b) For the input voltage shown in Fig 3. Determine the output if the input frequency is one kilohertz. (5 marks)

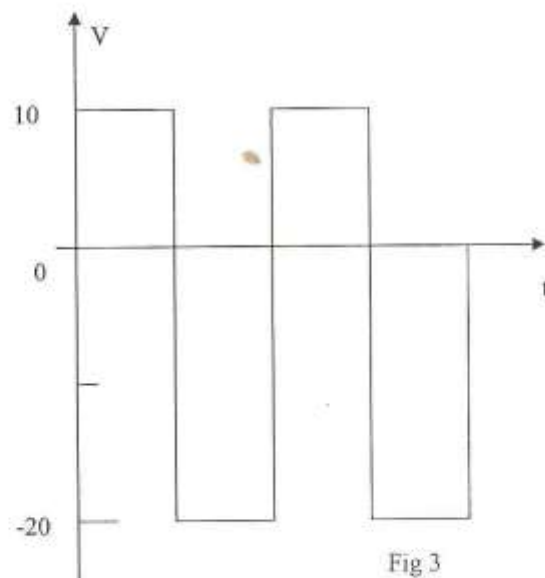

Question 5

For the circuit in Fig 4 $h_{fe}=200$, $h_{ie}=3200$ and $h_{oe}=20\mu\text{S}$

- (a) Draw the equivalent ac circuit of the amplifier.
- (b) Calculate the input impedance Z_i
- (c) Calculate the output impedance Z_o
- (d) Find the voltage gain A_v
- (e) Find the current gain A_i . (20 marks)

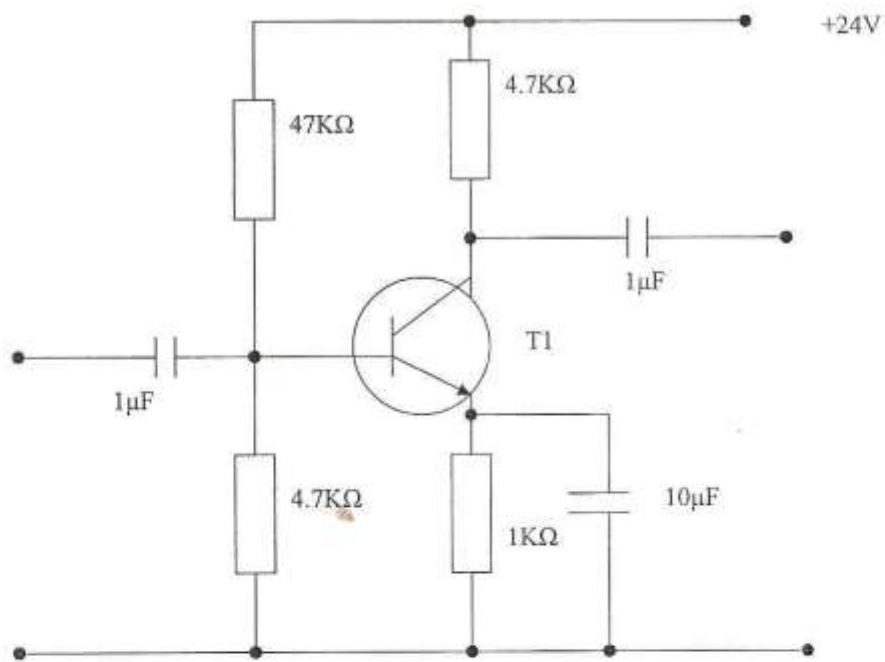


Fig 4

Question 6

- (a) For the FET in Fig 5 the $g_m = 3.4 \text{ mS}$ and $r_d = 100\text{K}\Omega$. Calculate the lower cut off frequency for the amplifier. (8 marks)

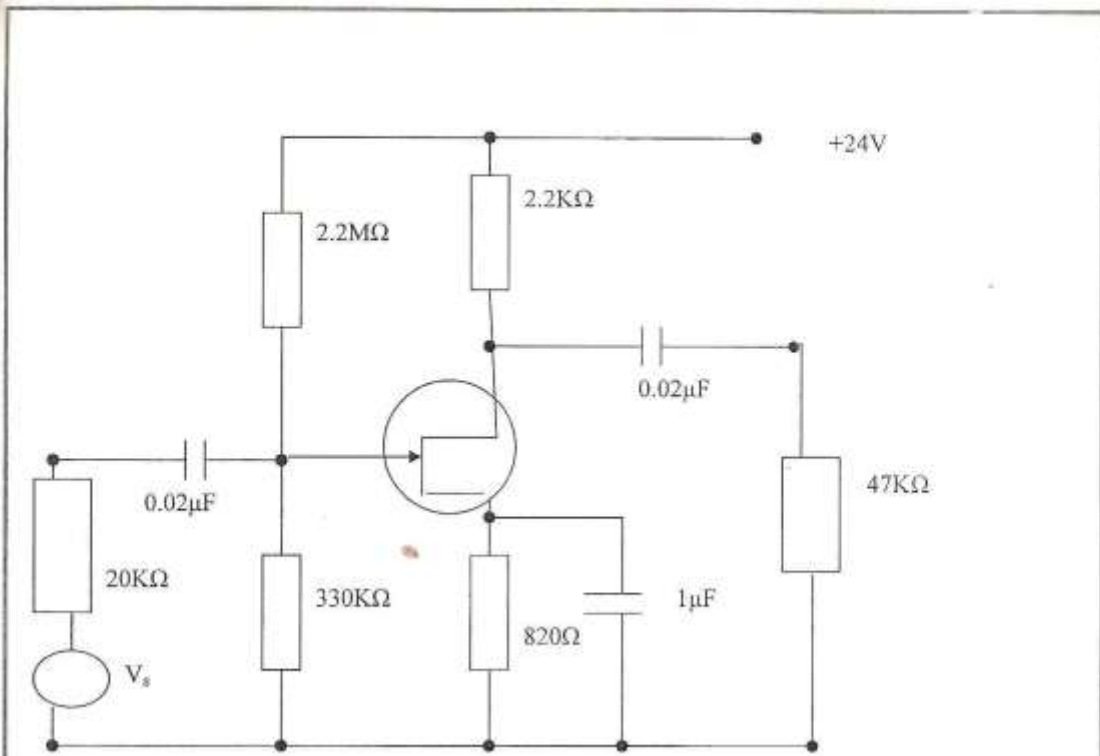


Fig 5

1

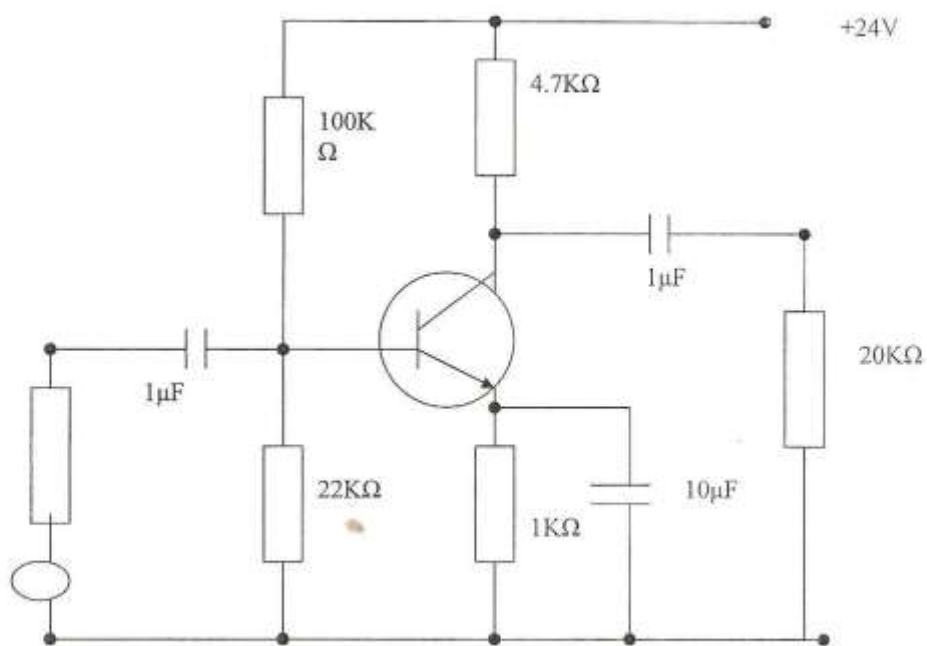


Fig 6

- (b) The transistor in figure 6 has a $\beta = 120$, $r_c = 20\Omega$, $r_o = 100K\Omega$ and $f_T = 100$ MHz. The inter electrode capacitances are $C_{be} = 40pF$, $C_{bc} = 1.5pF$ and $C_{ce} = 5pF$. The wiring capacitances across the input is $4pF$ and $8pF$ across the output. Determine the upper cut off frequency. (12 marks)

Question 7

- (a) Give four main features found in an IC voltage regulator. (4 marks)
- (b) A 78XX three terminal voltage regulator with external transistor and current limiting is used in a power supply, show the circuit connection of the regulator. (5 marks)
- (c) What is the function of a current mirror? Show the circuit arrangement of the current mirror. (6 marks)
- (d) Give five features that are achieved when using an amplifier with negative feedback. (5 marks)

Question 8

For the two stage amplifier in Fig 7 the β of T_1 is equal to 200 and of T_2 is equal to 100, while r_{e1} of the T_1 is $12\ \Omega$ and the r_{e2} for T_2 is $10\ \Omega$ and r_{c1} is $2M\Omega$.

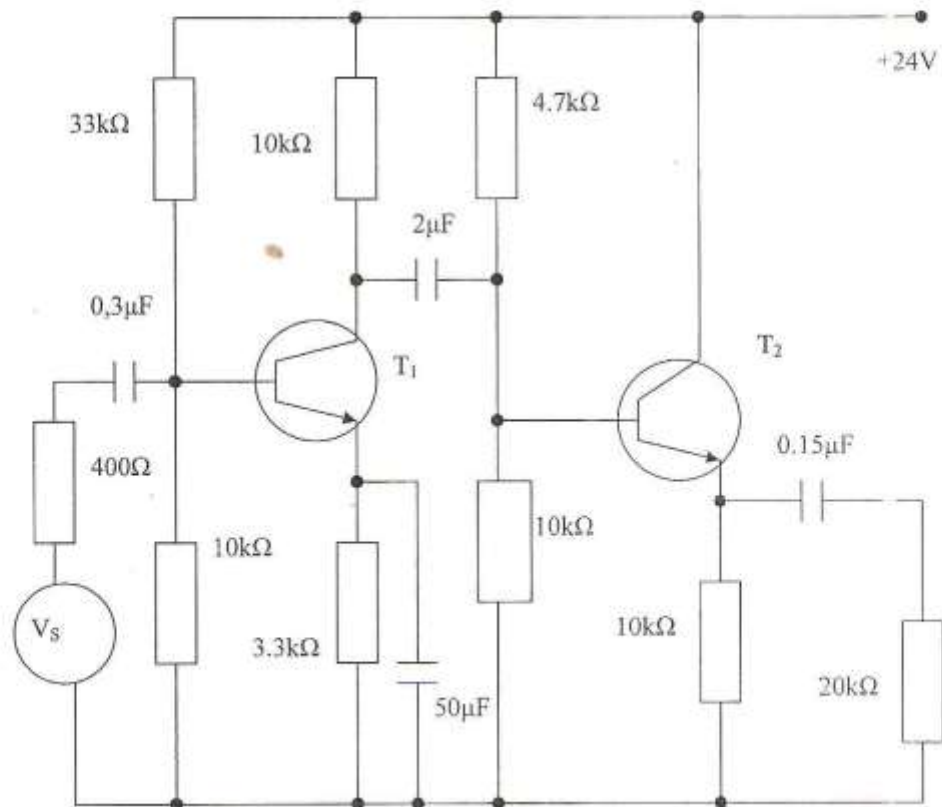


Fig 7

- Draw the equivalent ac circuit of the two stage amplifier.
- Calculate the voltage gain of the two stage amplifier.
- Calculate the current gain of the amplifier.
- Calculate the power gain of the amplifier. (20 marks)