

**NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY**  
**FACULTY OF INDUSTRIAL TECHNOLOGY**  
**BACHELOR OF ENGINEERING DEGREE**  
**DURATION 3 HOURS – JANUARY 2013**

**TEE 2111 DIGITAL ELECTRONICS**

**INSTRUCTIONS TO CANDIDATES**

1. ANSWER **ANY FOUR QUESTIONS ONLY**.
2. ALL QUESTIONS CARRY EQUAL POINTS.
2. SHOW YOUR STEPS CLEARLY IN CALCULATIONS
3. START THE ANSWER FOR EACH QUESTION ON A FRESH PAGE

**QUESTION ONE**

- (a) Convert the decimal number  $17983456_{10}$  into a straight code binary number. [4 points]
- (b) Using the method of borrowing subtract  $110011111_2$  from  $1001110000101_2$ . [6 points]
- (c) A logic function  $F = \Sigma (0, 3, 5, 8, 10, 11, 13, 15)$  is given.
  - (i) Write the expression for the function **F** in canonical form;
  - (ii) Minimize the expression using the Boolean algebra theorems;
  - (iii) Show how the minimized function can be implemented using 2-input NAND gates only. [15 points]

**QUESTION TWO**

- (a) Convert the octal number  $537146_8$  into a decimal and a binary number. [6 points]
- (b) Divide  $111011011101_2$  by  $1101_2$ . [6 points]
- (c) A logic function  $X = \Sigma (0, 1, 5, 6, 9, 10, 12, 14, 15)$ . Show how the function can be implemented using:
  - (i) 16-to-1 Multiplexer;
  - (ii) 8-to-1 Multiplexer;
  - (iii) 4-to-1 Multiplexer; [13 points]

**QUESTION THREE**

- (a) Convert the decimal number  $0.9734_{10}$  into a hexadecimal number. [4 points]
- (b) Use the 1s complement to subtract  $10101110010001_2$  from  $101001101_2$ . [6 points]
- (c) Show the circuit diagram for a 2-bit comparator implemented on 2-input NAND gates only. [15 points]

#### **QUESTION FOUR**

- (a) Convert the binary number  $11101100011011110010_2$  into a hexadecimal number. [3 points]
- (b) Use 2s complement to subtract  $11011001.011_2$  from  $110011101011101.1101_2$ . [6 points]
- (c) A logic function **E** is given, where  $\mathbf{E} = \Sigma ( 1, 2, 5, 7, 8, 9, 11, 14)$ .  
(i) Write the expression for the function  $\bar{\mathbf{E}}$ ;  
(ii) Minimize the expression using Boolean algebra theorems;  
(iii) Obtain an expression for the function **E** from the minimized  $\bar{\mathbf{E}}$ . [15 points]

#### **QUESTION FIVE**

- (a) Convert the decimal number  $38954_{10}$  into an octal number. [4 points]
- (b) Multiply  $101100110001_2$  by  $111010_2$ . [5 points]
- (c) A logic function  $\mathbf{U} = \Sigma (0, 2, 5, 7, 8, 9, 13, 14)$  is given. The 12 and 15 states are 'can't happen' states.  
(i) Using a Karnaugh map obtain a minimized expression for the function **U** from the function  $\bar{\mathbf{U}}$ ;  
(ii) Check the result using the method of 'perfect induction'. [16 points]

#### **QUESTION SIX**

- (a) Convert the binary number  $1100111011001_2$  into a decimal number. [5 points]
- (b) The binary numbers  $0111\ 0110\ 0101\ 0011_2$  and  $1000\ 1001\ 0111\ 1001_2$  are given in Binary Coded Decimal (BCD) code. Add the two numbers. [5 points]
- (c) Design a 4-input-and-one-output circuit, which is to implement the logic function **Y**. The function is logic '1' when there are only two '1's in the input code and logic '0' in all other cases:  
(i) From the truth table, derive an expression for **Y** and minimize it;  
(ii) Check your result using the method of 'perfect induction'. [15 points]