NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

FACULTY OF INDUSTRIAL TECHNOLOGY DEPARTMENT OF ELECTONIC ENGINEERING BACHELOR OF ENGINEERING (HONS) DEGREE

Final Examination January 2011

TEE 1103 ELECTRICAL ENGINEERING CIRCUIT ANALYSIS

Duration of Examination – 3 Hours

INSTRUCTIONS TO CANDIDATES

- 1. Answer any <u>FIVE</u> questions only.
- 2. Each question carries 20 marks.
- 3. Show your steps clearly in any calculation.
- 4. Start the answers for each question on a fresh page.

Question 1

Ţ

The Line w

For the network shown in figure 1,

a) Calculate the current through the $2k\Omega$ resistor.

[14 marks]

T

b) What is the voltage across, and the power dissipated in, the $2k\Omega$ resistor. [6 marks]



Figure 1.(All resistances are in Ohms and k denotes kilo)

1

ALE AND Question 2010011

For the network in figure 2:

E(CLEMER) (Using the format approach, write the nodal equations.

[9 marks]

[8-marks]

[3 marks]



c) Is the bridge balanced? Give reasons



Figure 2. (All resistances are in Ohms)

Question 3

For the circuit in Figure 3

- a) The capacitor is initially uncharged. Find mathematical expressions for the voltage across the capacitor, C₁, resistor R₁ and the current through the capacitor after the switch is thrown into position 1.
- b) After 6 time constants, the switch is thrown into position 2. Find mathematical expressions for the voltage across the capacitor, C₁, resistor R₂ and the current through the capacitor after the switch is thrown into position 2. [6 marks]
- c) Plot the waveforms for voltages and currents obtained in parts (a) and (b) on the same axis.

[8 marks]



Figure 3. (All resistances are in Ohms and k denotes kilo)

2

Question 4 For Figure 4,

atio

- Find the Thevenin's equivalent circuit for the network external to the 6Ω capacitive a) impedance. [14 marks]

nvenameresulting circulanton - Souton- commen



Figure 4(All impedances are in Ohms)

6 marks

[6 marks]

[3 marks]

Question 5

The network in figure 5 shows reactive and real power consumed by each block in an ac circuit.

- Find the total real, reactive and apparent power. a) [6 marks]
- Find the power factor. b) [2 marks]
 - Find the current I_T . c) [3 marks]
 - d) Draw the power triangle.
 - State the type of elements in each electrical box. e)



Question 6

For the circuit shown in figure 6, the frequency is 60Hz. (rk externala) Find the inductance of the 3 Ω impedance.

[3 marks]

b) Using Superposition Theorem, find the current through the 3Q impedance. [14 marks]



Figure 6. (All impedances are in Ohms)

END OF PAPER