

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY
FACULTY OF INDUSTRIAL TECHNOLOGY
BACHELOR OF ENGINEERING DEGREE
DURATION 3 HOURS – JANUARY 2011

TEE 2111 DIGITAL ELECTRONICS

INSTRUCTIONS TO CANDIDATES

1. ANSWER **ALL QUESTIONS**
2. SHOW YOUR STEPS CLEARLY IN CALCULATIONS
3. START THE ANSWER FOR EACH QUESTION ON A FRESH PAGE

QUESTION ONE

Convert the following numbers:

- a) 68780053_{10} into a binary number
- b) 12375401_8 into a hexa-decimal number
- c) 111010101010011.11101_2 into a decimal number
- d) 0.84765_{10} into an octal number
- e) $9DEC154_{16}$ into an octal number

[10 points]

QUESTION TWO

Perform the following binary arithmetic operations:

- a) Add 1010111101_2 and 11100111001_2
- b) Divide 100100111010010_2 by 110010_2
- c) Use 1s complements to subtract 1011011000101.101_2 from 10101100110.111_2
- d) Use 2s complements to subtract 10011001.11_2 from 11000111000111.101_2

[16 points]

QUESTION THREE

Redraw the circuit shown in Figure 1 using 2-input NAND gates only.

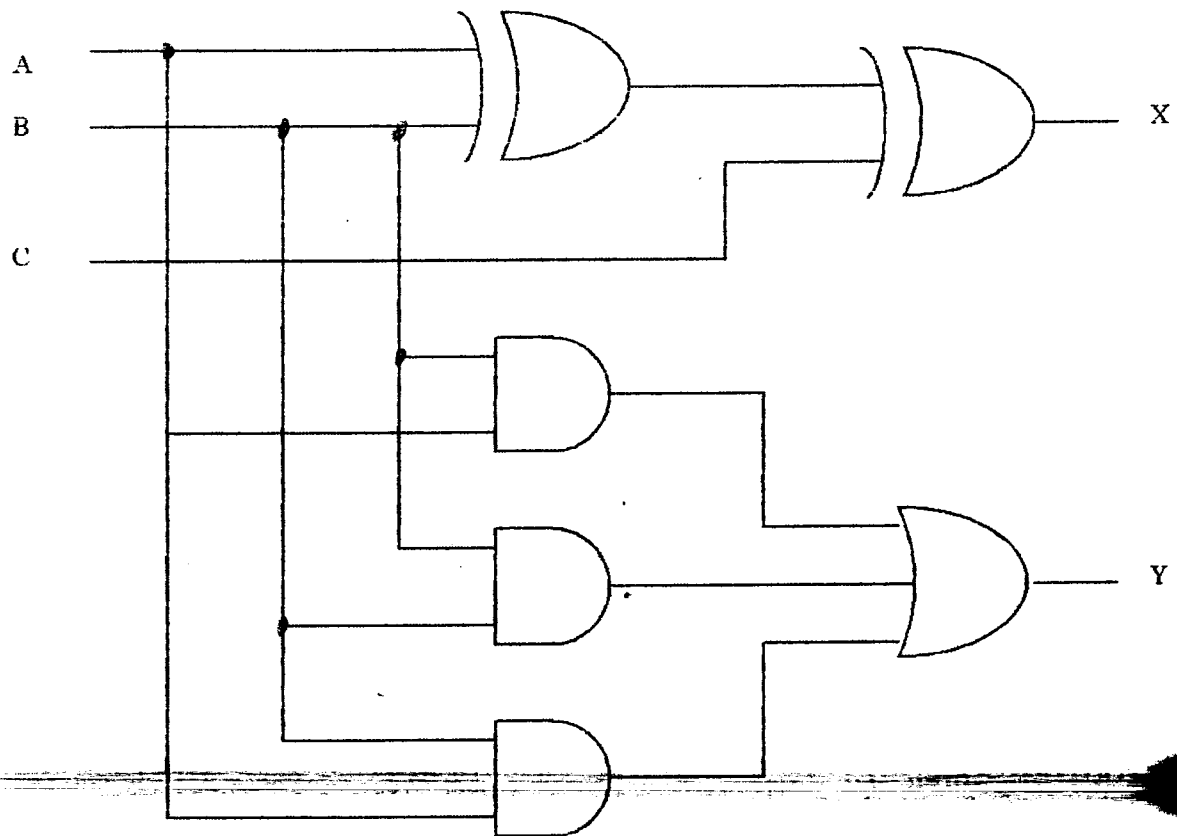


Figure 1

[8 points]

QUESTION FOUR

Consider the output **Y** in Table 1.

- Write the logic equation for the function **Y** as logic sum of AND terms
- Minimize the expression using Boolean algebra theorems.
- Convert the minimized expression from (c) so that the circuit is implemented on NOR gates only.
- Draw the circuit diagram

[20 points]

Table 1

A	B	C	D	Y	Z
0	0	0	0	1	0
0	0	0	1	1	1
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	1	1
0	1	0	1	0	0
0	1	1	0	1	X
0	1	1	1	0	0
1	0	0	0	1	1
1	0	0	1	0	X
1	0	1	0	1	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	1	X
1	1	1	0	0	0
1	1	1	1	1	1

QUESTION FIVE

Consider the output **Z** in Table 1.

- a) Write the logic equation for the function **Z** in canonical form.
- b) Transfer the expression for **Z** on a Karnaugh Map
- c) Minimize the expression.
- d) Convert the minimized expression from (c) so that the circuit is implemented on NAND gates only.
- e) Draw the circuit diagram.

[16 points]

QUESTION SIX

Using the circuit diagram of a full adder, show the full circuit diagram of an adder that will add two 3-bit numbers.

[10 points]

QUESTION SEVEN

A logic function **F** is given with the following expression:

$$F(A, B, C, D) = \Sigma(0, 1, 2, 4, 6, 8, 13, 14)$$

Use a 4-to-one multiplexer to implement the logic function

[10 points]

QUESTION EIGHT

Design a binary-to-octal decoder circuit. Only one output at time should be at logic 1 indicating the binary code at the inputs. Draw the circuit diagram.

[10 points]