

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

FACULTY OF INDUSTRIAL TECHNOLOGY

BACHELOR OF ELECTRONIC ENGINEERING (HONS) DEGREE

Supplementary Examination August
2011 TEE 2111

Analogue Electronics

Duration of Examination 3 Hours

Instructions to Candidates:

1. Answer any **five** questions only.
2. All questions carry equal marks.
3. Show all your steps clearly in any calculation.
4. Start the answers for each question on a fresh page.

Question 1

- (a) The circuit values in figure 1 are $R_1=33\text{ k}\Omega$, $R_2=10\text{ k}\Omega$, $R_C=2.2\text{ k}\Omega$, $R_E=1\text{ k}\Omega$ and $V_{CC}=18\text{ V}$. A silicon NPN transistor is used with $\beta=100$. Find the base working current I_{BQ} , the collector working current I_{CQ} and the collector emitter working voltage V_{CEQ} .

(15 marks)

- (b) A thermistor is used for temperature stabilization ,what type of thermistor would it be .
.Re-draw the circuit with the thermistor .

(5 marks)

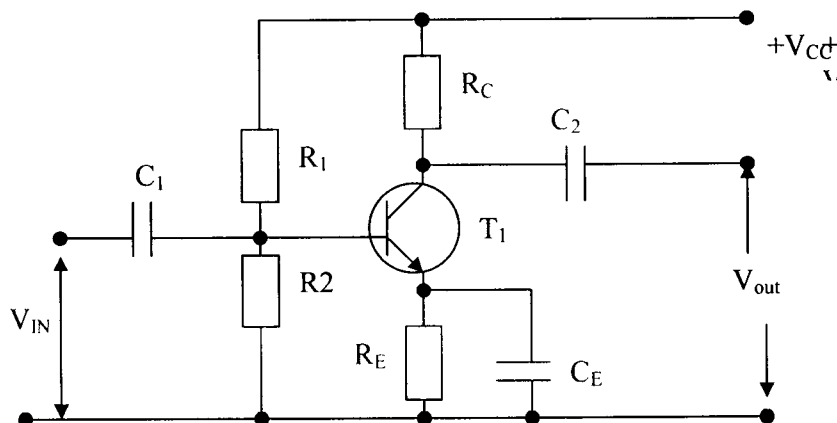


Fig 1

Question 2

For the feedback amplifier shown in fig 2 assume that $A_v=100$ determine:

- (i) the overall voltage gain of the amplifier
 - (ii) the input impedance Z_{if}
 - (iii) the output impedance Z_{of}
 - (iv) What effect if any does the negative feedback has on the bandwidth of an amplifier.
- (20 marks)

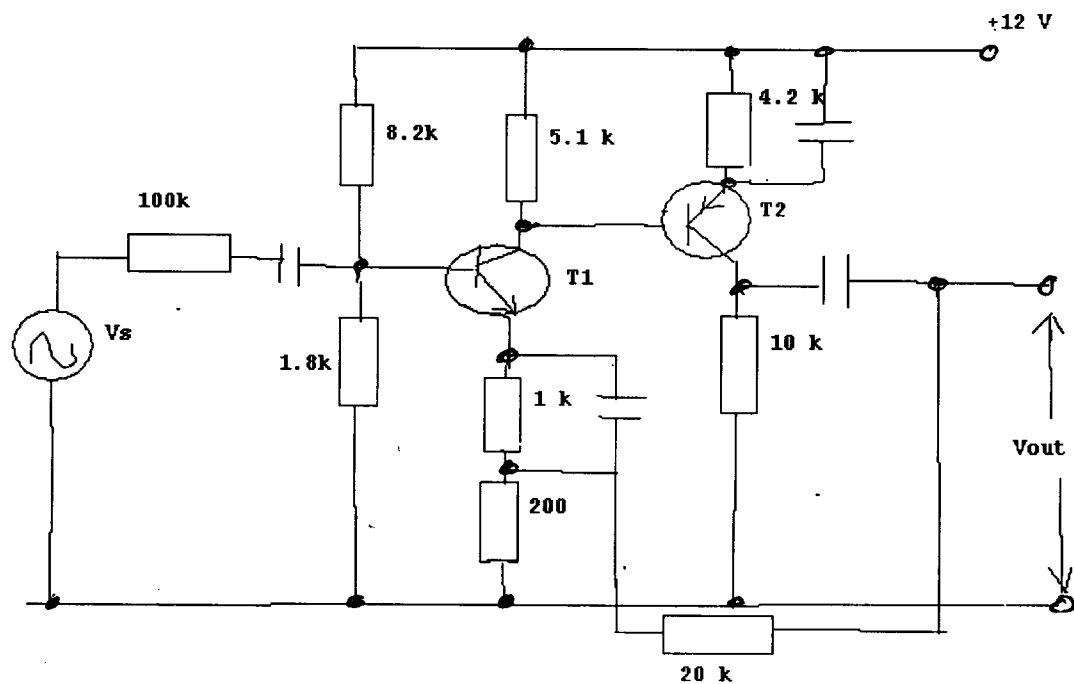


Fig 2

Question 3

For the circuit shown in fig 3

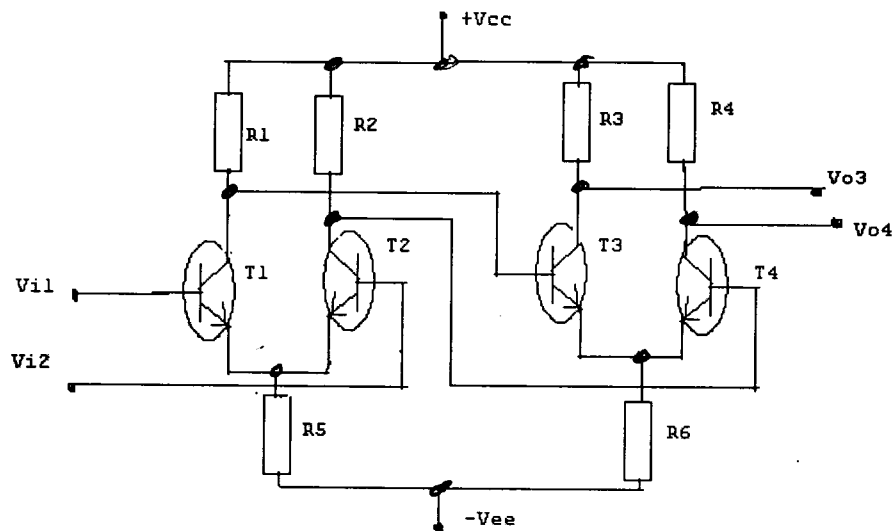


Fig 3

- Draw the half equivalent circuit that would be used to calculate the differential voltage gain. (6 marks)
- Give the expression that would be used to find the differential input resistance. (2 mark)
- Give the expression used to calculate the differential voltage gain. (4 marks)
- Draw the half equivalent circuit that would be used to find the common mode equivalent circuit. (6 marks)
- Give the expression of the common mode input resistance for the circuit. (2 marks)

Question 4

In integrated circuit techniques the following circuits are used. Show the arrangement of each circuit when used.

- Level shifting with emitter follower. (4 marks)
- Voltage level-shifting with zener diode (4 marks)
- Temperature compensated bias circuit. (4 marks)
- Current mirror circuit. (4 marks)
- Current source circuit which is not temperature dependent. (4 marks)

Question 5

- (a) Draw the circuit diagram of a basic step up and a basic step down switching regulator. For each circuit give the expression for the output voltage. (10 marks)
- (b) Determine the minimum and the maximum output voltage for the LM317 regulator shown in

Figure 4 below given that $I_{ADJ} = 100\mu A$

(6 marks)

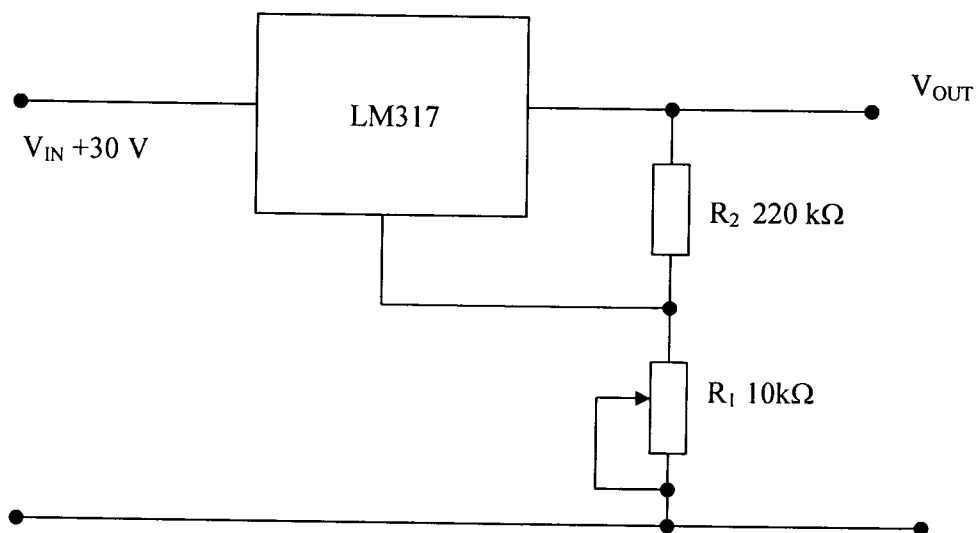


Fig 4

- (c) A 78XX series three terminal regulator with external transistor and current limiting is used in a power supply, show the circuit connection of the regulator. (4 marks)

Question 6

With the help of characteristics differentiate between the output and transfer characteristics of a MOSFET in the depletion mode, enhancement mode use some numerical values in your characteristics Draw the circuit symbol of each MOSFET. (20 marks)

Question 7

(a) Find the current I_1 in the circuit in fig 5.

(4 marks)

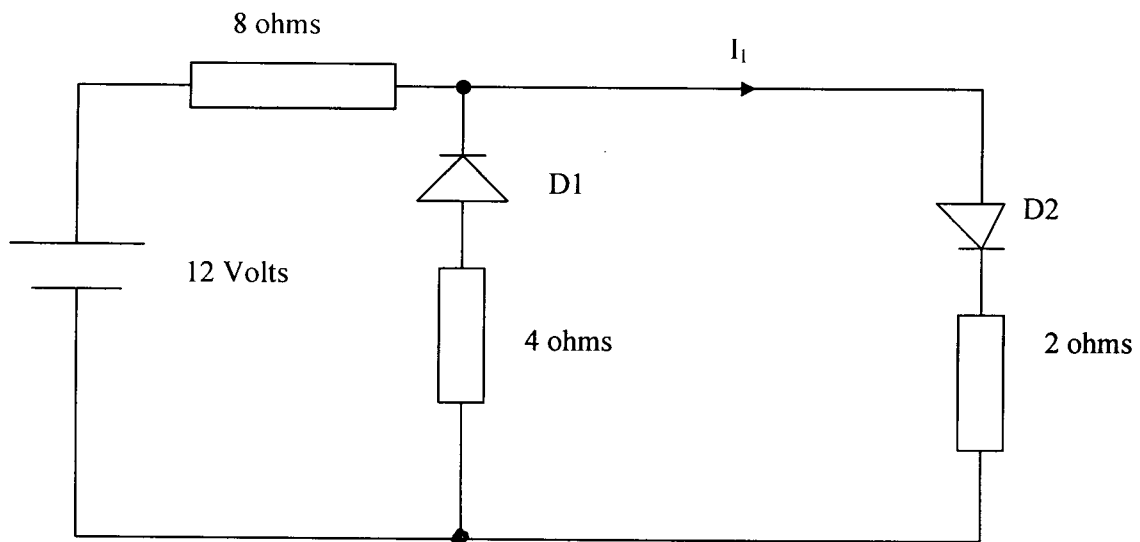


Fig 5

(b) A 80 volts peak to peak ac voltage supplies the input of the circuit

in fig 6 .Sketch the output waveform at the point marked V_{OUT} .(4marks)

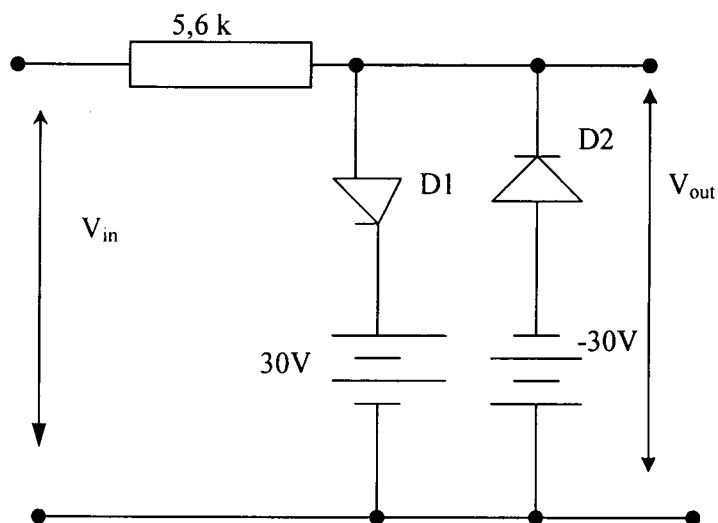
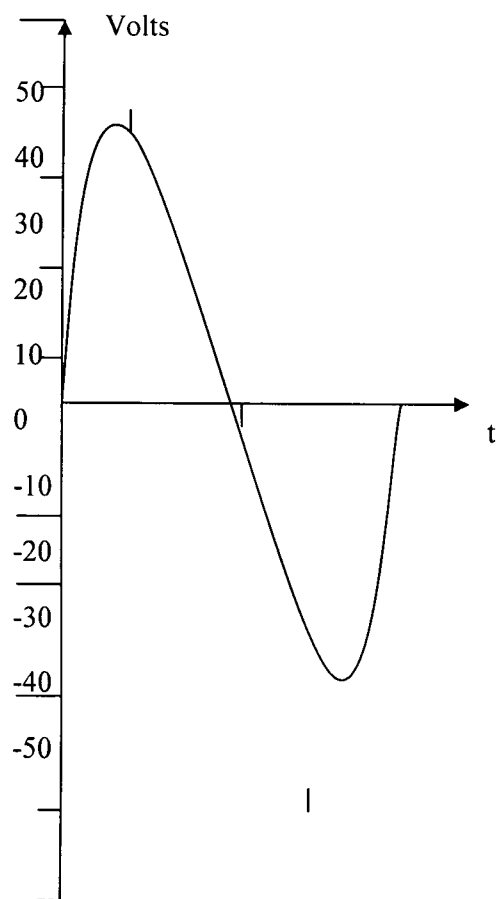


Fig 6

(c) Design a circuit that will produce the output waveform that is shown at the output of the black box when a the shown waveform is applied at the input terminals in fig 7. What is the name of the circuit designed. (6 marks)

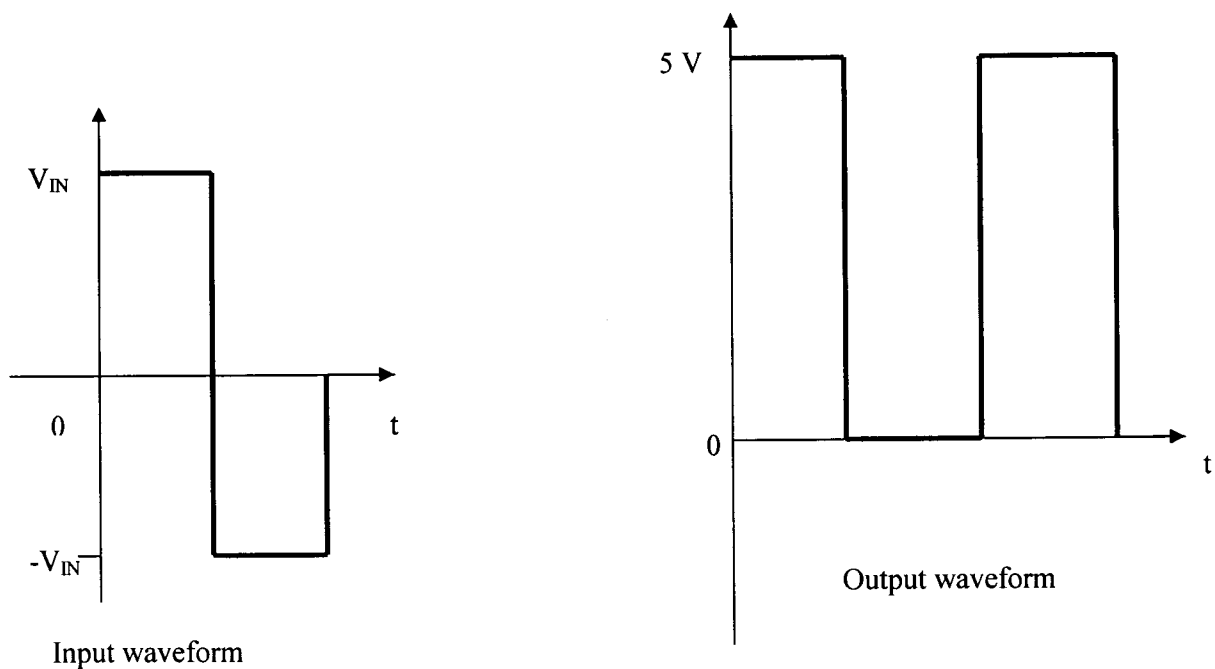


Fig 8

- (e) State the names of two materials that are mostly used in making semiconductors. (2 marks)

Question 8

- (a) Draw a typical circuit that can be used as a CMOS gate. (5 marks)
- (b) For an N-channel JUGFET I_{DSS} is 9 ma, V_P is minus 3,5 Volts and V_{GS} is minus 2 Volts. For the JUGFET calculate the value of the drain current I_D , the value of g_{mo} and the value of g_m . (5 marks)
- (c) A zener diode is used with a series resistor $R_s = 20$ ohms, $V_Z = 18$ Volts and a load resistor of $R_L = 200$ ohms. Draw the circuit of the stabilized power supply. The input varies from 20 Volts to 30 Volts.
- (i) Calculate the minimum and the maximum currents of the zener diode (3 marks)
- (ii) Determine the minimum and the maximum power that is

dissipated in the zener diode .

(3 marks)

(iii) The minimum rated power dissipation in the series resistor R_s ... (4 marks)