

NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY
FACULTY OF INDUSTRIAL TECHNOLOGY
BACHELOR OF ENGINEERING DEGREE
ADVANCED INTEGRATED CIRCUITS AND MICROELECTRONICS – TEE 5111
SUPPLEMENTARY EXAMINATION – AUGUST 2011
DURATION 3 HOURS

INSTRUCTIONS TO CANDIDATES

1. ANSWER **ANY FOUR** QUESTIONS
2. EACH QUESTION CARRIES EQUAL MARKS
3. SHOW YOUR STEPS CLEARLY IN CALCULATIONS
4. START THE ANSWER FOR EACH QUESTION ON A FRESH PAGE

Q. 1.

- a) Describe the characteristics of an operational amplifier classified as 'Low Noise'.
[4 points]
- b) Explain the procedure in integrated circuits fabrication called 'Oxidation'.
[8 points]
- c) Show the circuit diagram of a Widlar Current Source. Give the relationship between the input and the output current.
[6 points]
- d) Give the block diagram of a Basic Isolation Amplifier. Explain its operation.
[7 points]

Q. 2.

- a) Describe the characteristics of an operational amplifier classified as 'Low Drift'.
[4 points]
- b) Explain the procedure in integrated circuits fabrication called 'Zone Refining'.
[6 points]

- c) Show the circuit diagram of a Simple Current Source. Give the relationship between the input and the output current.

[6 points]

- d) A SiO₂ layer of 0.4 μm is to be grown on (100) silicon by dry oxidation at temperature of 1000 °C. Find the time required using the information below.

$$x_o = \frac{A}{2} \left[\sqrt{1 + \frac{t + \tau_o}{A^2/4B}} - 1 \right], \text{ where } \tau_o = \frac{x_i^2 + Ax_i}{B};$$

$$t = \frac{A^2}{4B} \left[\left(\frac{2x_o}{A} + 1 \right)^2 - 1 \right] - \tau_o, \quad A = K_1 e^{+E_1/kT} \quad \text{and} \quad B = K_2 e^{-E_2/kt}$$

Parameter	(111) Silicon		(100) Silicon	
	Wet	Dry	Wet	Dry
K ₁ (μm)	2.39.10 ⁻⁶	1.24.10 ⁻⁴	4.02.10 ⁻⁶	2.08.10 ⁻⁴
K ₂ (μm ² /hour)	214	772	214	772
E ₁ (eV)	1.29	0.77	1.29	0.77
E ₂ (eV)	0.77	1.23	0.71	1.23
x _i (μm)	0	0.02	0	0.02

$$k = 8.63.10^{-5} \text{ eV/}^\circ\text{K}$$

[9 points]

Q. 3.

- a) Describe the characteristics of an operational amplifier classified as 'Wide-band'.

[4 points]

- b) Explain the procedure in integrated circuits fabrication called 'Photolithography'.

[8 points]

- c) Show the circuit diagram of a level – shifter circuit using a Voltage Multiplier. Give the relationship between the input and the output voltage.

[6 points]

- d) Give the circuit diagram of an Instrumentation Amplifier and derive expression for its voltage gain.

[7 points]

Q. 4.

- a) Describe the characteristics of an operational amplifier classified as 'High Current'.

[4 points]

- b) Explain the procedure in integrated circuits fabrication called 'Diffusion'.

[7 points]

- c) Show the circuit diagram of an R/2R ladder Digital – to – Analogue Converter. Use equivalent circuits to prove the circuit operation for the following conditions:

D ₀	D ₁	D ₂	D ₃
1	1	0	1
0	0	1	1
0	0	1	0
1	1	0	1

Assume that the logic 1 (high level) is 5 V.

[14 points]

Q. 5.

- a) Describe the characteristics of an operational amplifier classified as 'High Voltage'.

[4 points]

- b) Explain the procedure in integrated circuits fabrication called 'Crystal Growth'.

[5 points]

- c) Show the circuit diagram of a Multiple Current Source. Explain the practical application of a such source.

[6 points]

- d) Give circuit diagram, illustrate and explain the principle of operation of:

- (i) A Voltage to Frequency Converter;
- (ii) A Frequency to Voltage Converter.

[10 points]

Q. 6.

- a) Describe the characteristics of an operational amplifier classified as 'Low Bias Current'.

[4 points]

- b) Explain the procedure in integrated circuits fabrication called 'Metalization'.

[6 points]

- c) Show the circuit diagram of a level – shifter circuit using a Darlington Pair. Give the relationship between the input and the output voltage.

[7 points]

- d) Show the circuit of a Differential Amplifier as a monolithic integrated circuit. Derive an expression for:
- The differential close-loop voltage gain
 - The common-mode voltage gain.

[8 points]