



NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

FACULTY OF APPLIED SCIENCES

DEPARTMENT OF APPLIED PHYSICS

BSc (Hon) in EARTH SCIENCE PART 1

ELECTRIC CIRCUITS AND INSTRUMENTATION

SPH 1107

First Semester Examination Paper

December 2024

This examination paper consists of 4 pages

Time Allowed: 3 hours

Total Marks: 100

Special Requirements: None

Examiner's Name: Mr Z. Zulu

INSTRUCTIONS


ANSWER ALL PARTS OF QUESTION 1 IN SECTION A AND ANY THREE QUESTIONS FROM SECTION B. SECTION A CARRIES 40 MARKS AND SECTION B CARRIES 60 MARKS.

MARK ALLOCATION

QUESTION	MARKS
1.	40
2.	20
3.	20
4.	20
5.	20
6.	20
Maximum possible mark	100


SECTION A

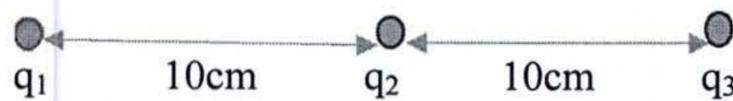1. (a) State the properties of a point charge [3]
- (b) State 4 uses of an Op- amp in an electronic circuit. [5]
- (c) (i) State the significance of the time constant in RC circuits. [2]
(ii) Calculate the time constant τ of a circuit with resistor of 10Ω and capacitance of $5\mu\text{F}$. [5]
- (d) State the following Laws [4]
(i) Kirchhoff's voltage law [4]
(ii) Kirchhoff's current law [3]
(iii) Faraday's Law of induction [3]
(iv) Coulomb's law [3]
- (f) From the diagram below, calculate the force on charge q_3 given that $q_1 = +3\mu\text{C}$, $q_2 = -2\mu\text{C}$ and $q_3 = 1\mu\text{C}$



[7]

(g)

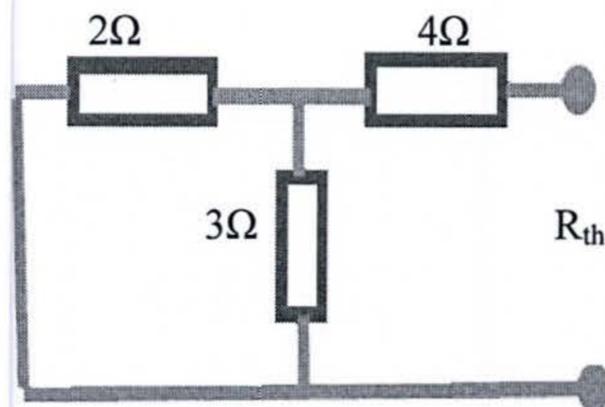


Calculate the thevenin resistance of the circuit above.

[5]


SECTION B

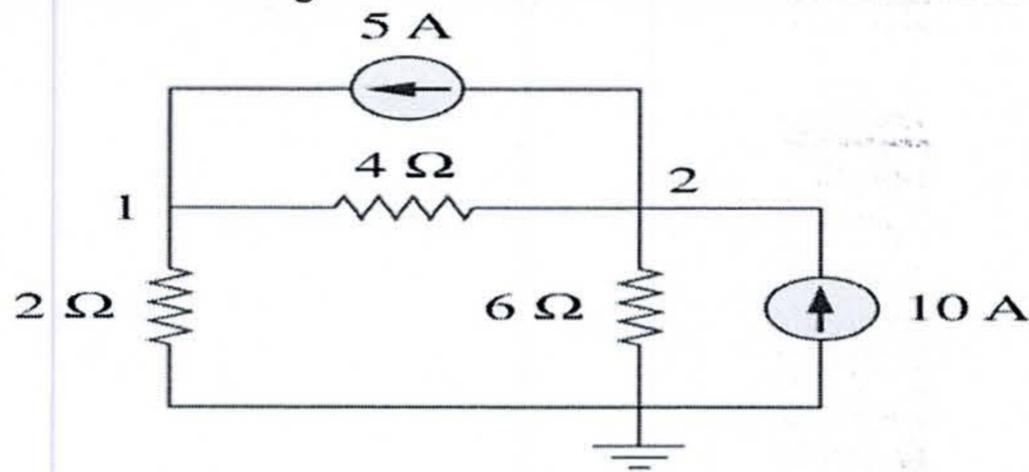2. (a) Draw symbols to show an independent voltage source and a dependent voltage source [4]
- (b) Use source transformation technique to transform the following sources [3]
- (i) 8mA source with a $5k\Omega$ resistor [3]
- (ii) 15V source [3]
- (c) Calculate the nodal voltages at the two numbered nodes in the circuit below.



[10]

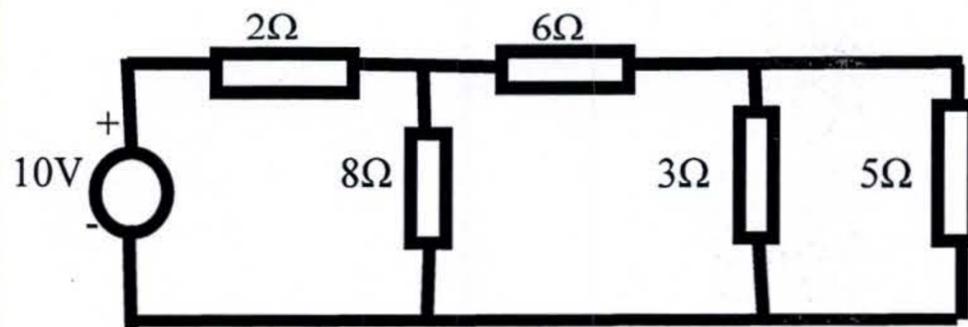
3. (a) State any two properties of an op-amp. [2]
- (i) State any two uses of an op-amp. [4]
- (ii) Draw a diagram to show a voltage follower and state its gain. [4]
- (b) Using Kirchoff's laws give 5 equations formed from analyzing the circuit below.



[10]

4. (a) Calculate the value equivalent to [4]
- (i) 2F, 3F and 4F capacitors connected in series [4]
- (ii) 2H, 3H and 4H Inductors connected in series [2]
- (b) Draw the symbol for a BJT transistor. [2]
- (c) Derive the period of motion T of a particle in a Cyclotron and show that it is dependent only on the magnetic field B , the mass m and charge q of the particle. [10]

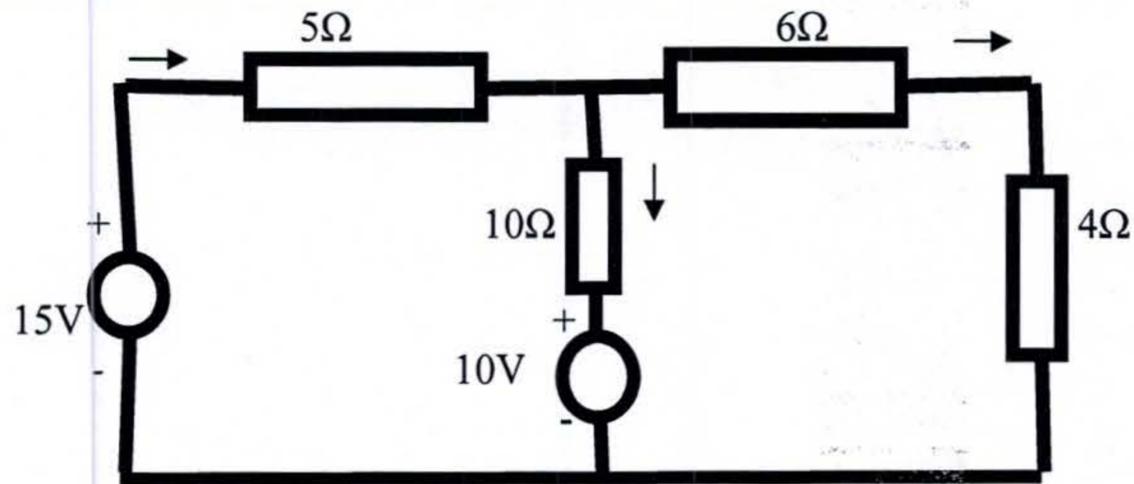5. (a) State the factors affecting the value of capacitance. [4]
 (b) Give Maxwell's equations stating each parameter in them. [8]
 Calculate the value of the three currents in the circuit below



[8]

6. (a) State two uses of capacitors. [4]
 (b) Calculate the energy and charge stored in a 3pF capacitor connected to a 20V power supply. [6]
 (c) State the difference between first order and second order circuits and draw one second order circuit [10]

END OF PAPER