



**NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY  
FACULTY OF APPLIED SCIENCES  
DEPARTMENT OF COMPUTER SCIENCE**

**FUNDAMENTALS OF DIGITAL ELECTRONICS  
SCS 1112**

**Examination Paper**

**December 2024**

This examination paper consists of 3 pages

**Time Allowed:** 3 hours  
**Total Marks:** 100  
**Examiner's Name:** MR. SIBANGISO NGWENYA  
**External Examiner:** DR CROSS GOMBIRO

**INSTRUCTIONS**

1. Answer any four (4) questions
2. Each question carries 25 marks

**MARK ALLOCATION**

<b>QUESTION</b>	<b>MARKS</b>
1.	25
2.	25
3.	25
4.	25
5.	25
<b>TOTAL FOR ANY FOUR QUESTION</b>	<b>100</b>

### QUESTION ONE

- a) Differentiate between serial-in serial-out and parallel-in parallel-out shift registers. Give examples. [5]
- b) Construct a 4-bit shift register using D flip-flops and explain its working. [5]
- c) Discuss the S-R flip-flop and draw a truth table that corresponds to it. [5]
- d) Describe the operation of a 4-bit shift register. Include a timing diagram for a right shift operation. [10]

### QUESTION TWO

- a) List out any 2 advantages of using digital circuitry. [2]
- b) Differentiate between synchronous and asynchronous counters. [3]
- c) Discuss the applications of shift registers in digital systems. [5]
- d) Discuss the uses and limitations of the S-R latch. [5]
- e) Construct an S-R latch using NAND gates. [10]

### QUESTION THREE

- a) Perform the following binary operations
  - i.  $1011000_2 - 111000_2$  [5]
  - ii.  $1000100_2$  from  $1011000_2$  [5]
- b) Explain the concept of two's complement and demonstrate how to find the two's complement of the binary number 1010. [5]
- c) Explain the working principle of a binary encoder. Draw the truth table for an 8-to-3 encoder. [10]

#### QUESTION FOUR

- a) Describe a demultiplexer and explain how it differs from a multiplexer with a suitable example. [5]
- b) If the output of a circuit is high (1) when both inputs are low (0), identify the type of gate and justify your answer with a truth table. [10]
- c) Define a multiplexer and explain its working with a 4-to-1 multiplexer circuit diagram. [10]

#### QUESTION FIVE

- a) What is the difference between an encoder and a decoder? Provide examples. [5]
- b) Simplify the following Boolean expression using Boolean algebra:  
 $F(A,B,C) = A.B + A.B' + A'.C$  [10]
- c) Discuss the importance of binary arithmetic in digital electronics. [10]

**END OF QUESTION PAPER**

