

	NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY FACULTY OF ENGINEERING DEPARTMENT OF ELECTRONIC ENGINEERING ELECTRICAL ENGINEERING CIRCUIT ANALYSIS EEE 1143
	Examination Paper December 2024

This examination paper consists of 5 pages

Time Allowed: 3 hours

Total Marks: 100

Special Requirements: N/A

Examiner's Name: Mr B. Dlodlo & Ms S. Nyathi

INSTRUCTIONS

1. Answer ALL questions
2. Use of calculators is permissible
3. Begin each answer to a full question on a fresh page.

MARK ALLOCATION

QUESTION	MARKS
A1.	6
A2.	9
A3.	10
A4.	9
A5.	8
A6.	9
A7.	9
B1.	20
B2.	20
TOTAL	100

Copyright: National University of Science and Technology, 2024

SECTION A (Answer all questions)**QUESTION A1**

Define the following terms,

- a) Voltage. [2]
 b) Current. [2]
 c) Resistance. [2]

QUESTION A2

Using Mesh analysis, determine the current through R_2 in the network of figure QA2. [9]

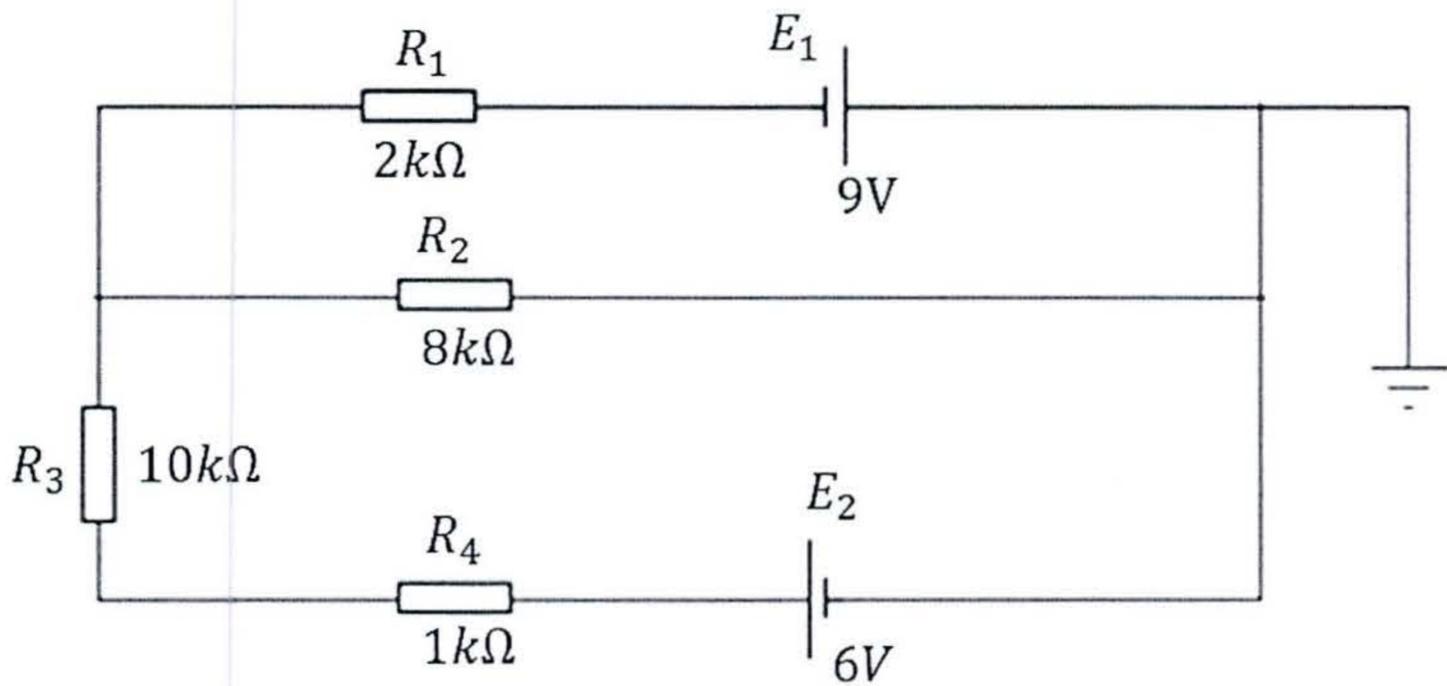


Figure QA2

QUESTION A3

For the network shown in figure QA3,

- a) Find the Thevenin's equivalent circuit for the network external to the resistor R . [7]
 b) State the value of R for maximum power transfer. [1]
 c) Calculate the value of the power dissipated in R at maximum power condition. [2]


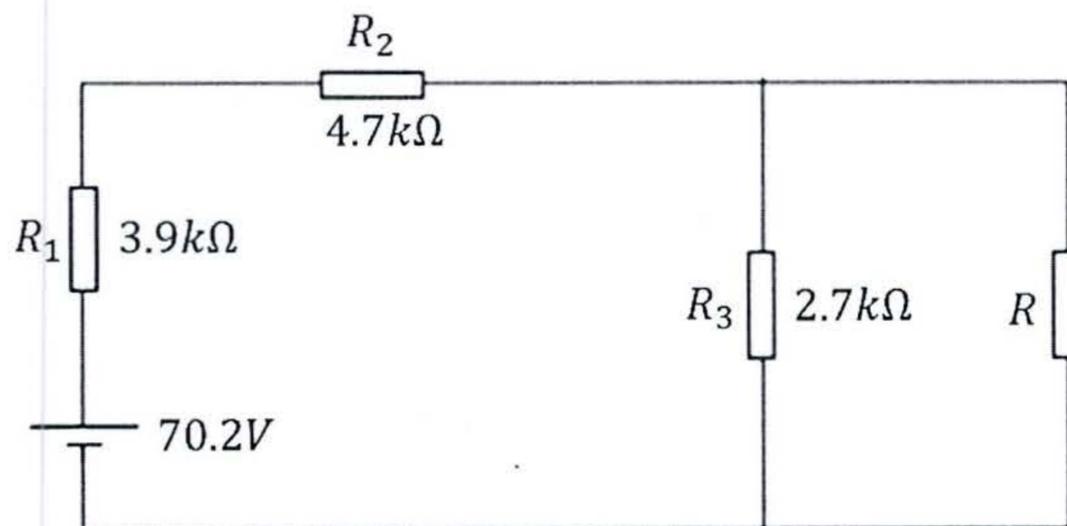


Figure QA3

QUESTION A4

Using the Superposition Theorem in the network of figure QA4, find the current through the resistor R_1 . [9]

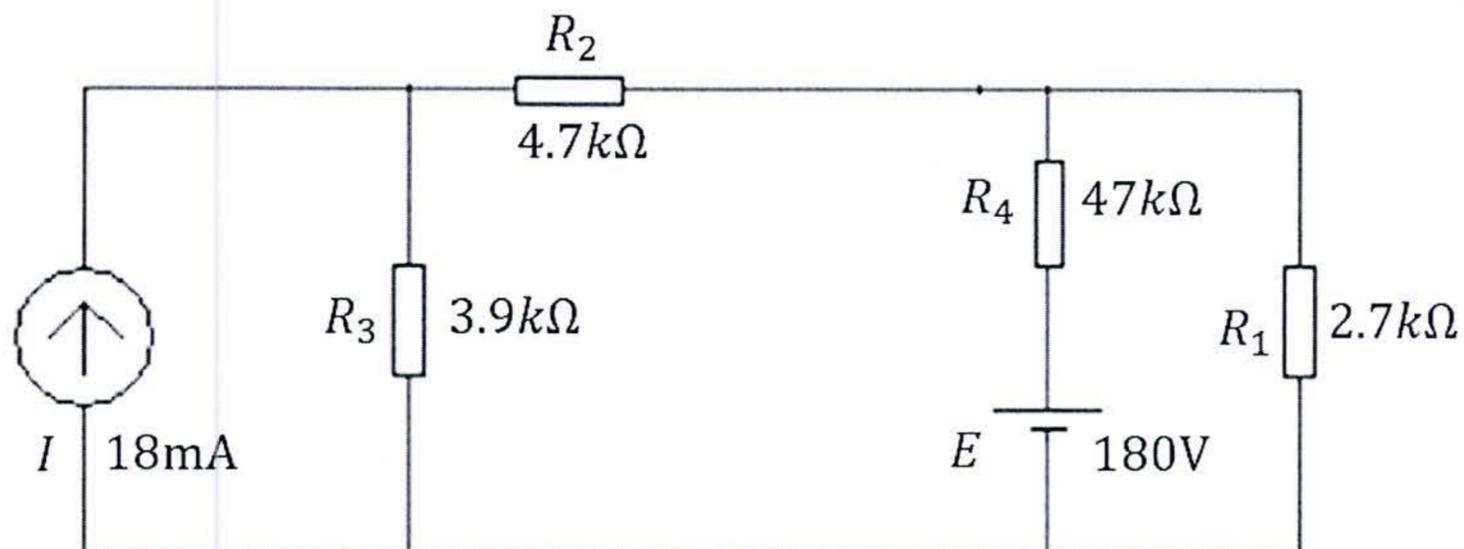

FigureQA4

QUESTION A5

Consider the circuit shown in figure QA5. The capacitor is initially uncharged. The switch is closed at time, $t = 0$ ms. Determine the time it takes for the capacitor to charge to 19V. [8]

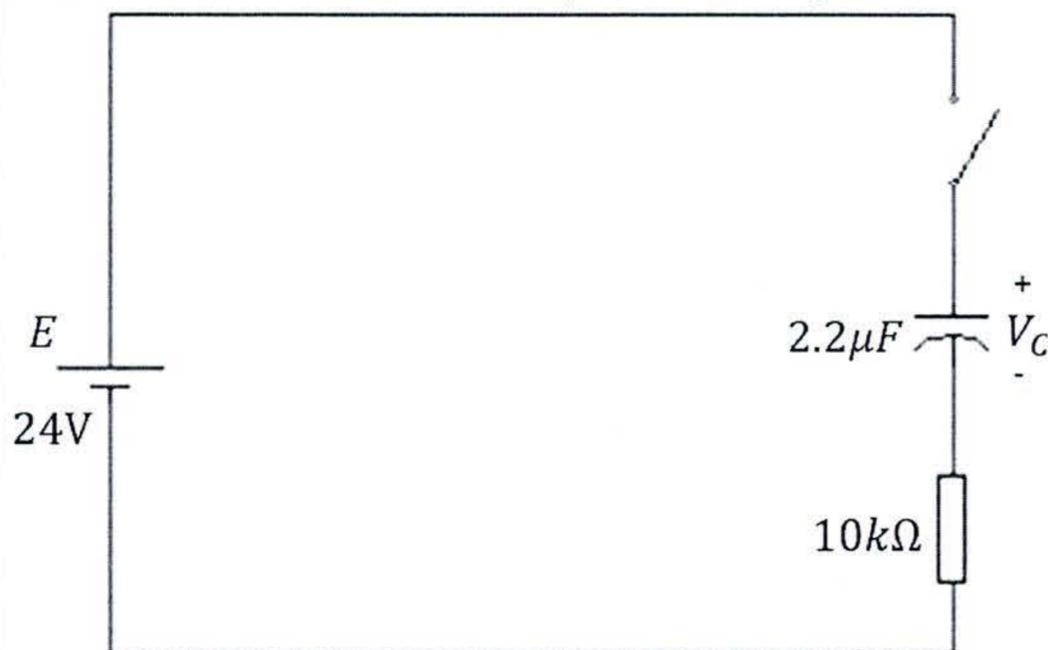


Figure QA5

QUESTION A6

In the magnetic circuit of figure QA6, the total core length is 0.2m, the air gap length is 8×10^{-4} m, and the cross-sectional area is 2×10^{-4} m². The coil has 500 turns. Magnetic fringing may be ignored. The relative permeability of cast steel may be taken to be 680. Permeability of free space is given as $4\pi \times 10^{-7}$ H/m.

- Draw the magnetic equivalent circuit. [2]
- Determine the current required to establish a flux density of 0.8T in the air gap. [5]
- Calculate the magnetic field strength in the core. [2]

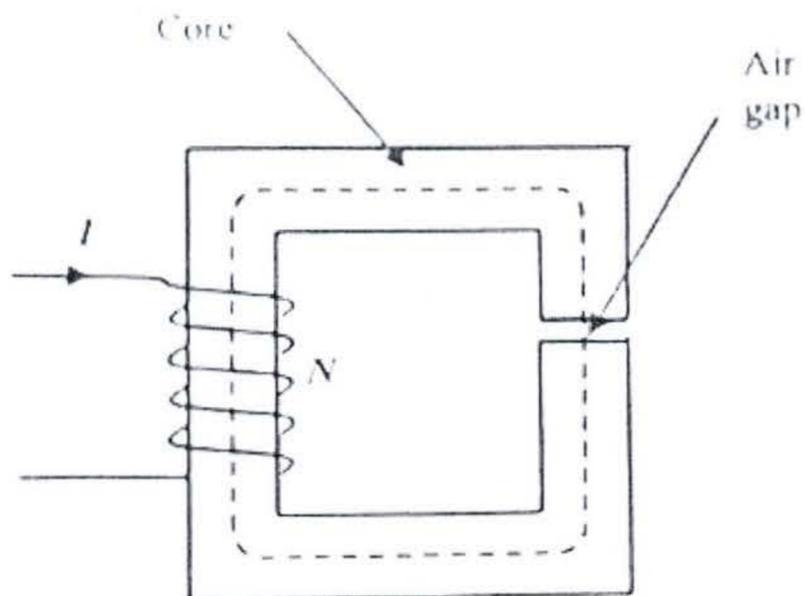


Figure QA6

QUESTION A7

For the network of figure QA7,

- Calculate the total apparent power and overall power factor. [4]
- Calculate the total current drawn from the source. [2]
- Sketch the waveforms for supply voltage and source current on the same axes. [3]

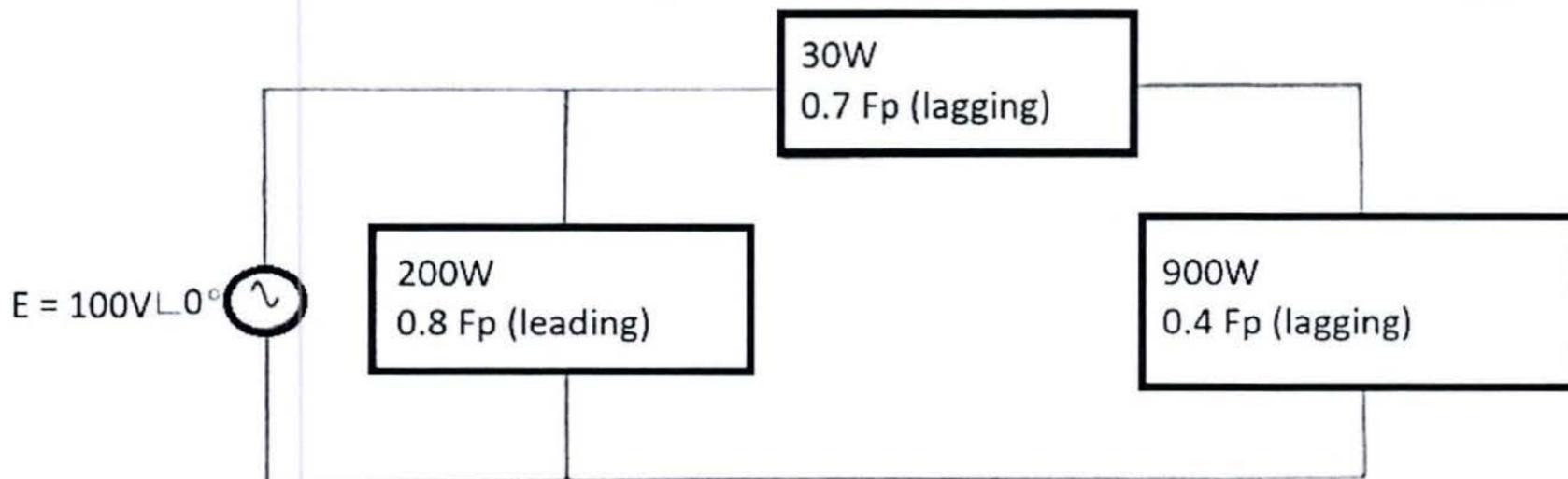


Figure QA7

SECTION B (Answer all questions)**QUESTION B1**

For the network shown in figure QB1,

- Obtain the total resistance as seen by the source. [14]
- Calculate the conductance as seen by the source. [2]
- Calculate the current drawn from the source. [2]
- Determine the voltage drop across R_{int} . [2]

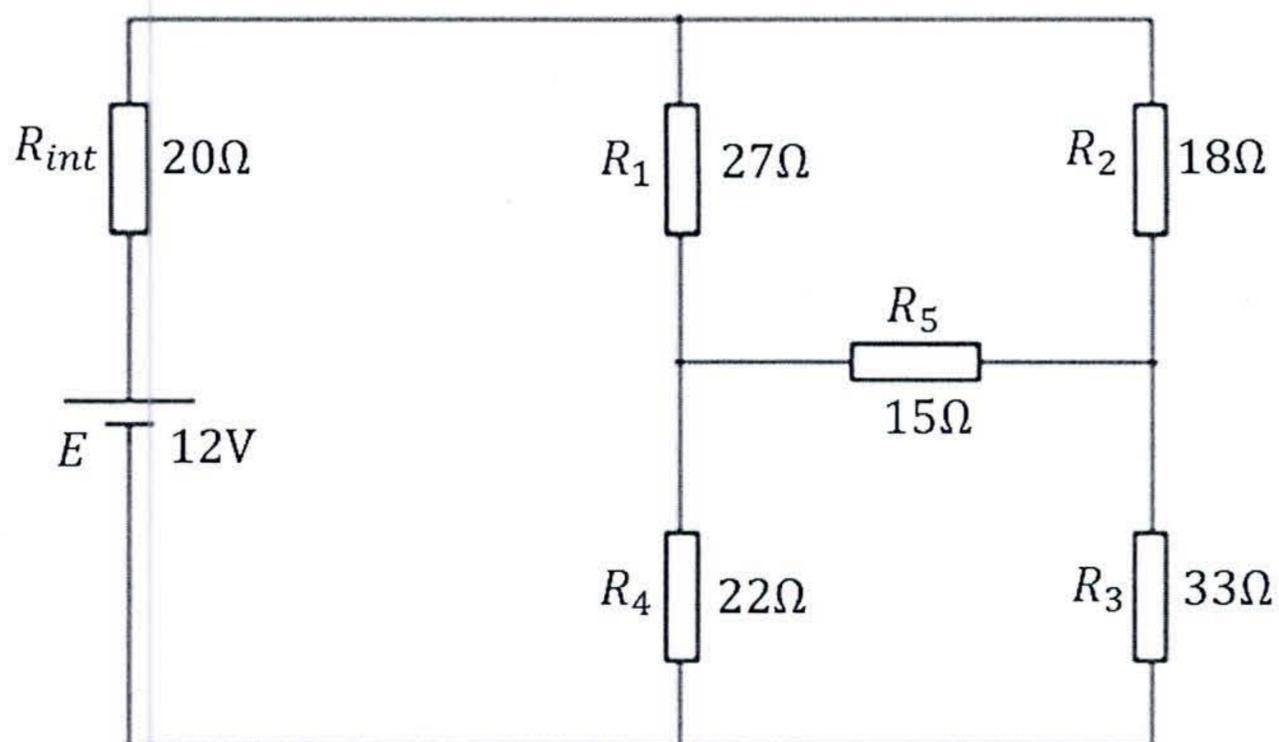


Figure QB1

QUESTION B2

For the network shown in figure QB2, determine I_5 , I_8 and V_8 .

[20]

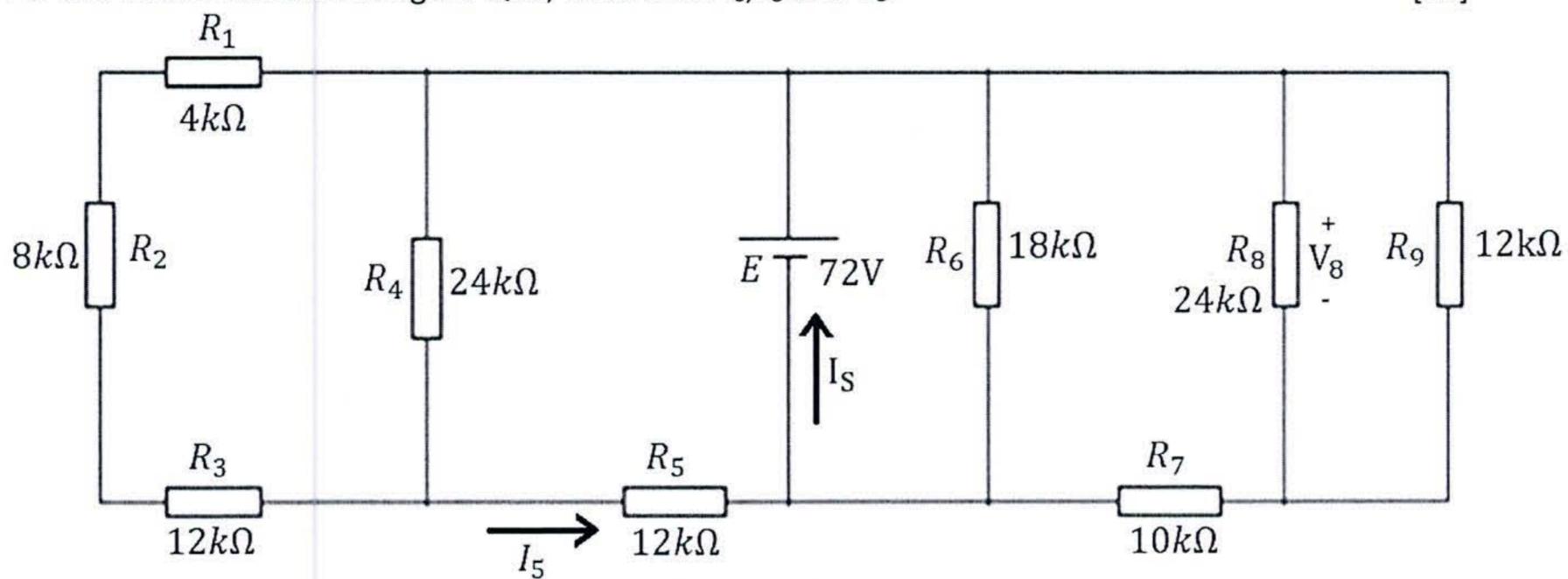


Figure QB2

END OF THE PAPER