



NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY

FACULTY OF ENGINEERING

DEPARTMENT OF ELECTRONIC ENGINEERING

**ELECTRONIC ENGINEERING CIRCUITS AND DEVICES
EEE 1203/EEE 1213**

**FINAL EXAMINATION PAPER
JULY 2024**

This paper consists of 7 printed pages.

EXAMINATION DURATION : **3 HOURS**
TOTAL MARKS : **100**
SPECIAL REQUIREMENTS : **None**
EXAMINER'S NAME : **FUNANI. J**

INSTRUCTIONS TO CANDIDATES

- i. Answer **ALL** questions in **Section A** and **any THREE** from **Section B**
- ii. Each question in **Section B** carries **20 marks**.
- iii. Show any calculations and assumptions clearly.
- iv. Start each question on a fresh page.

Boltzman constant = $1.381 \times 10^{-23} \text{ J/K}$
eV = $1.602 \times 10^{-19} \text{ J}$

SECTION A

Answer Multiple Choice Questions 1 – 10 on the same page.

- 1. The concentration of current carriers in an intrinsic semiconductor:**
 - A. Is constant over a large temperature range
 - B. Decreases exponentially with increase in temperature
 - C. The current carriers' concentration depends on the type of semiconductor material only
 - D. Increases exponentially with increase in temperature
- 2. An N- type semiconductor is obtained by:**
 - A. Inserting atoms of elements of valence III between semiconductor atoms
 - B. Adding elements of valence III to an intrinsic semiconductor
 - C. Converting the bonds between the atoms from covalent to ionic bonds
 - D. Replacing some of the semiconductor atoms with atoms of an element of valence IV
- 3. At room temperature, the current in an intrinsic semiconductor is due to**
 - A. Holes and electrons
 - B. Electrons
 - C. Ions
 - D. Holes
- 4. Which of the following inserts a DC level in a waveform?**
 - A. Clipper
 - B. Clamper
 - C. Amplifier
 - D. Limiter
- 5. In a Zener diode large reverse current is due to**
 - A. Collision
 - B. Presence of impurities
 - C. Rapture of bonds
 - D. Lower resistance in reverse biased region
- 6. Which of the following diodes is operated in reverse bias mode?**
 - A. P-N junction
 - B. Zener
 - C. Tunnel
 - D. Schottky
- 7. Which of the following components adds or restores a DC level to an electric signal?**
 - A. Clamper
 - B. Clipper
 - C. Diode
 - D. Transistor
- 8. The equation that gives the relationship between the currents in a bipolar junction transistor (BJT) is**
 - A. $I_C = I_E + I_B$
 - B. $I_B = I_E + I_C$
 - C. $I_E = I_B - I_C$
 - D. $I_E = I_C + I_B$
- 9. A Bipolar Junction Transistor (BJT) mode of operation when both the Emitter junction (EJ) and the Collector junction (CJ) are reverse biased:**
 - A. Is called the 'saturation mode'


- B. A BJT does not allow both (EJ) and (CJ) to be reverse biased.
- C. Is called the 'cut-off' mode of operation
- D. Is called 'inverse active' mode of operation

10. In common collector (cc) configuration the input and output parameters are:

- A. Input: I_B and V_{CE} ; Output: I_E and V_{CE}
- B. Input: I_E and V_{BE} ; Output: I_B and V_{CE}
- C. Input: I_B and V_{CB} ; Output: I_C and V_{CB}
- D. Input: I_C and V_{CB} ; Output; I_B and V_{CB}

11. Draw the output waveform produced by the circuit below


[3]

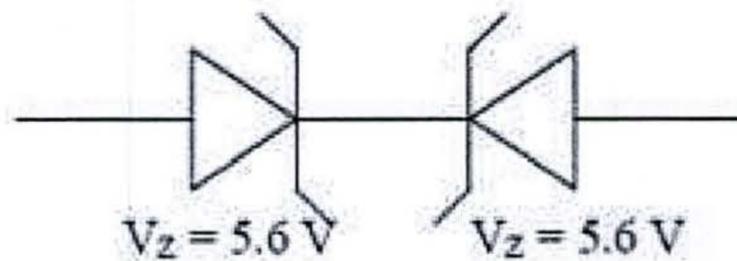

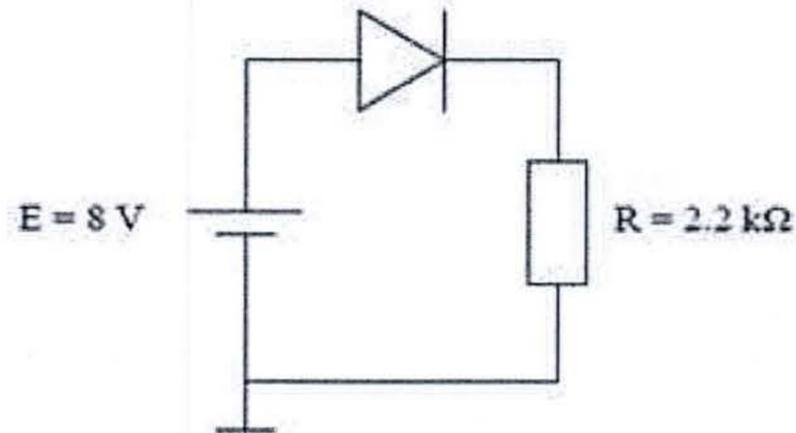- 12. Differentiate between drift current and diffusion current with respect to semiconductor materials** [2]
- 13. With the aid of an energy band diagram, explain the difference between a metal, semiconductor and insulator in terms of the energy band diagram.** [6]
- 14. Explain with suitable diagrams the formation of PN junction** [2]
- 15. Explain the behavior of a P junction when forward biased** [4]
- 16. Explain the behavior of a PN junction when reverse biased** [3]

SECTION B

- B111 For the circuit shown below, determine the current through and the voltage across the resistor R and the voltage across the diode. Assume Si diode. [4]




- B112 With reference to BJT transistor operating regions, complete the following table with relevant information [10]

| | Bias mode | Emitter Junction (EJ) | Collector Junction (CJ) |
|----------|-----------|-----------------------|-------------------------|
| Cutoff | | | Reverse |
| | | Forward | Reverse |
| Inverted | | Reverse | |
| | | Forward | Forward |

- B113 A transistor has the following currents: $I_E = 15\text{mA}$, $I_B = 60\mu\text{A}$, calculate: [6]
- α_{dc}
 - β_{dc}

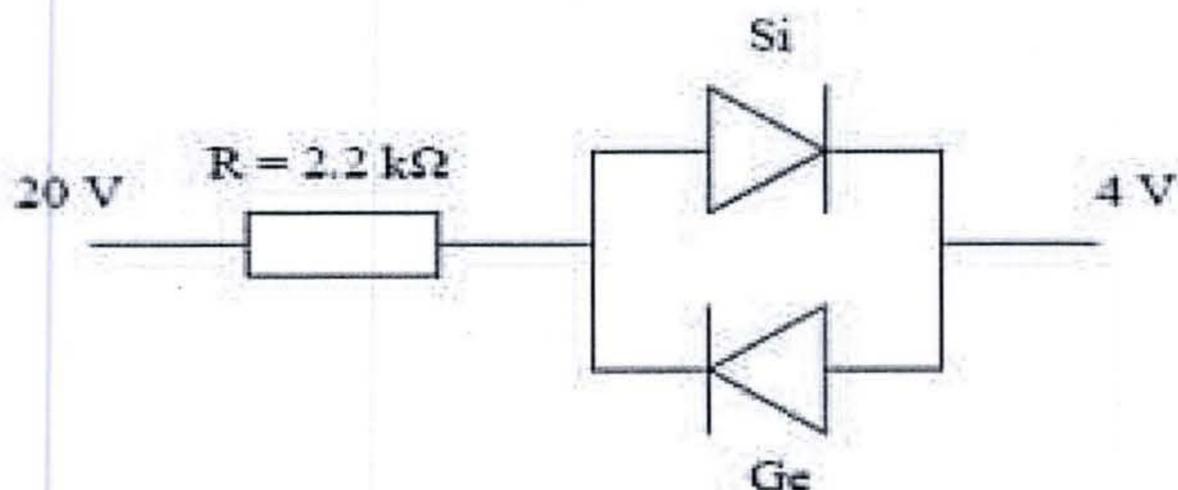
- B211 Determine the current through the Resistor r for the circuit below [4]



B212 Given the NPN transistor in CB configuration mode, with $\beta = 100$ shown below, calculate


[8]

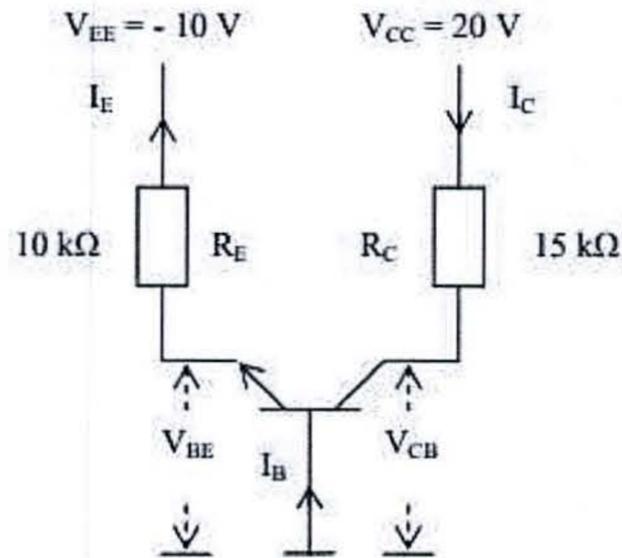- i. I_E
- ii. I_C
- iii. V_{CB}
- iv. I_B



B213 Determine the current through and the voltage across each component for the circuit below


[8]

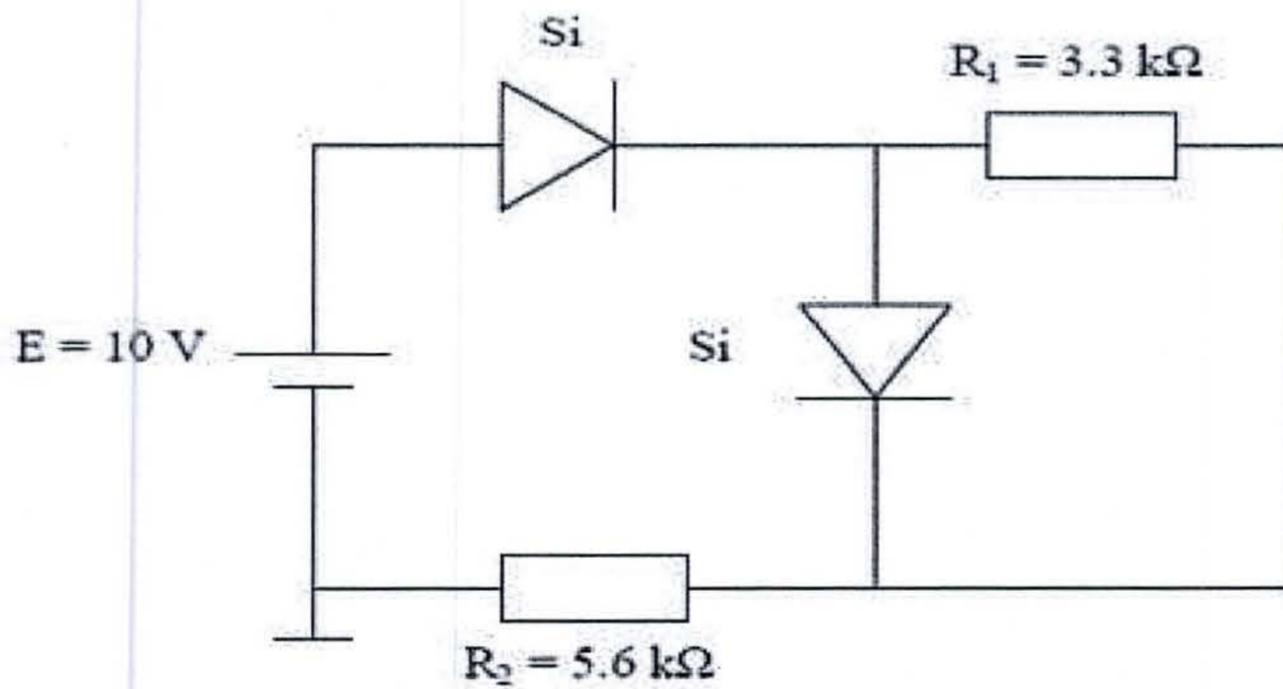

B311 For the circuit below, calculate


[6]

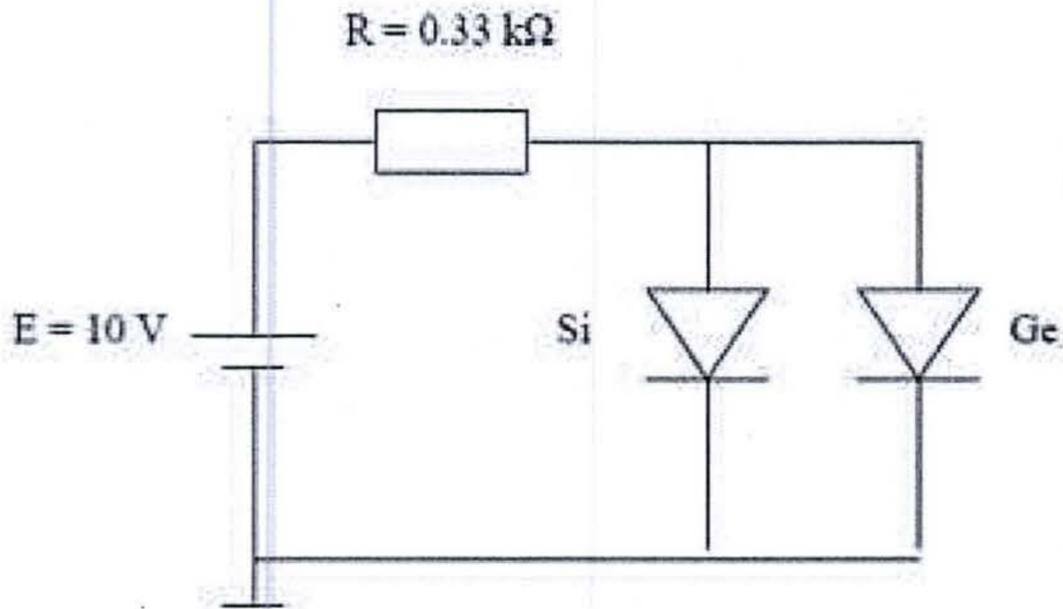- i. The total current and the currents through the Si and the Ge diodes.
- ii. The total current through the diodes if all the diodes were Si




B312 Given a Si diode with a reverse current (I_R) of 35nA at 25°C, calculate its reverse current at 100°C. [4]

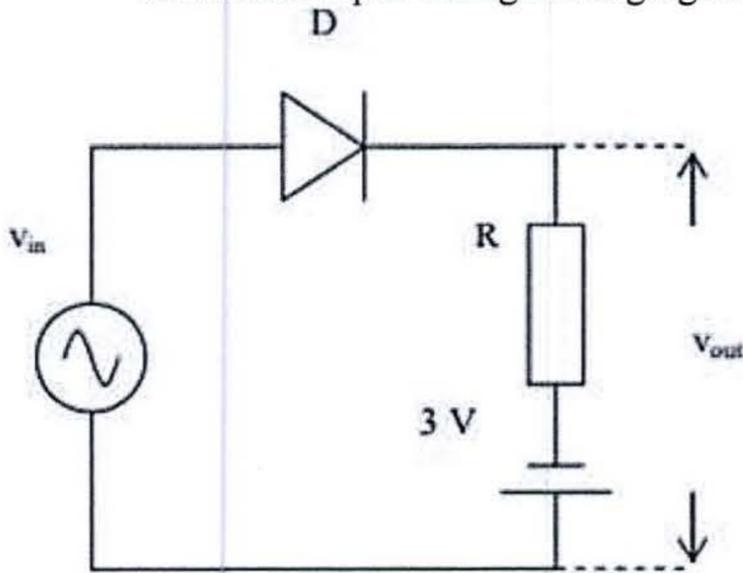
B313 For the clipper circuit below
 i. Identify the name of the clipper
 ii. Explain how the circuit works and draw the output waveform considering a sinusoidal input voltage swinging from -10 to +10 and an ideal diode [10]



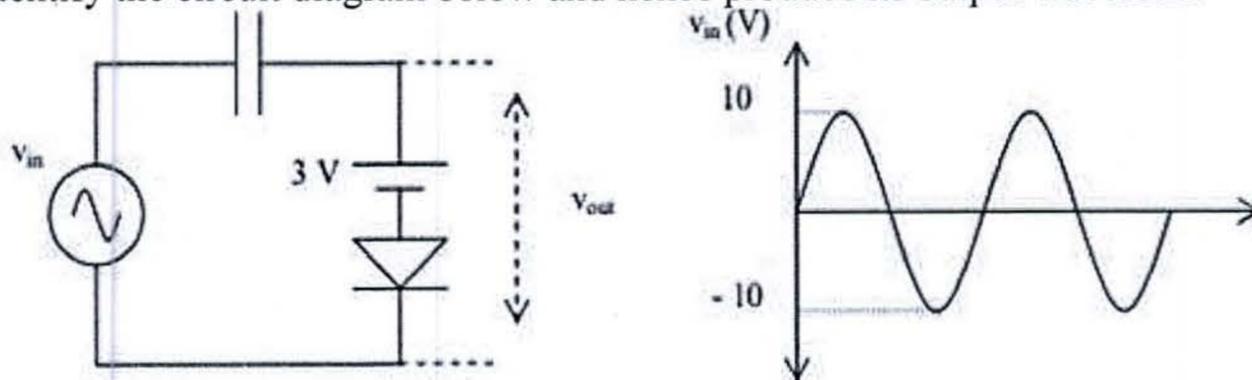B411 Identify the circuit diagram below and hence produce its output waveform [6]



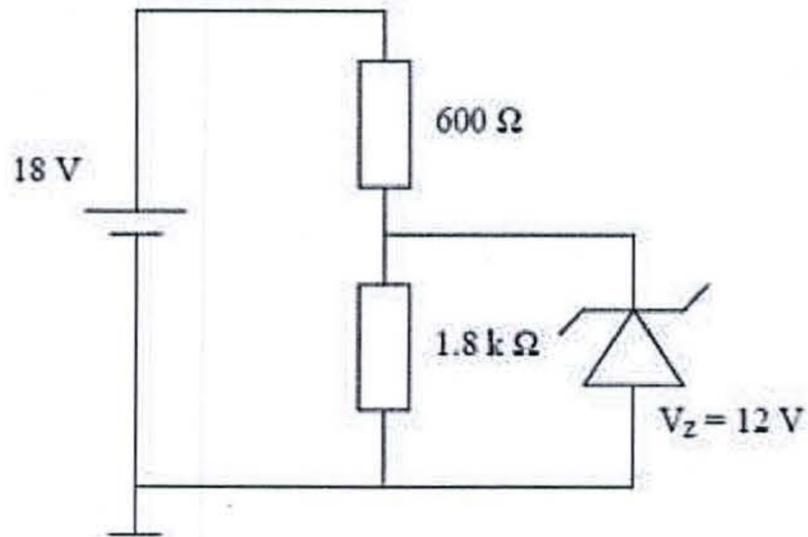
B412 Calculate the current through each resistor and zener diode [6]



B413 Draw the block diagram of a power supply and explain each block [8]

B511 For the voltage divider bias configuration shown below, determine: [10]

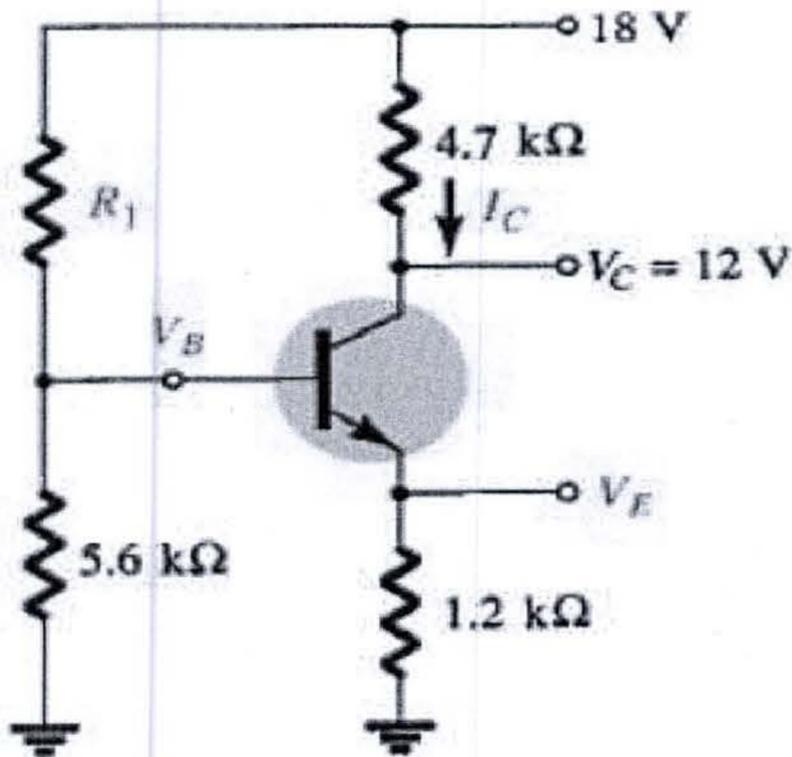- i. I_C
- ii. V_E
- iii. V_B
- iv. R_1
- v. $I_{C(sat)}$



B512 Define a rectifier [1]

B513 Draw a full wave bridge rectifier circuit, explain its operation and draw its output waveform. [9]