



NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY
FACULTY OF ENGINEERING
ELECTRONIC ENGINEERING DEPARTMENT
DIGITAL ELECTRONICS
EEE 1214

Examination Paper
September 2024

This examination paper consists of 3 pages

Time Allowed: 3 hours

Total Marks: 100

Examiner's Name: Nondo John W

INSTRUCTIONS

1. Answer All Questions
2. Start the answer for each question on a fresh page

MARK ALLOCATION

QUESTION	MARKS
1.	20
2.	20
3.	20
4.	20
5.	20
TOTAL	100

Copyright: National University of Science and Technology, 2021

Question 1

Perform the following conversions:

- 1.1 Convert the straight code binary 11001100011101.11011_2 number into decimal number. [4 points]
- 1.2 Convert the decimal number 631728_{10} into the straight code binary number. [4 points]
- 1.3 Convert the straight code binary number 111011100110001110110_2 into:
 - a. Octal number;
 - b. Hexadecimal number.[4 points]
- 1.4 Convert the hexadecimal number $AC9052_h$ into decimal number. [4 points]
- 1.5 Convert the decimal number 0.9872_{10} into octal number. [4 points]

Question 2

Perform the following arithmetic operations:

- 2.1 Add the straight code binary numbers 1100101111_2 , 10100110011_2 and 111011001100_2 . [4 points]
- 2.2 Use the 1s complement subtraction method to subtract the straight code the binary number 1010101_2 from 10000011_2 . [4 points]
- 2.3 Use the 2s complement subtraction method to subtract the straight code the binary number 1110000_2 from 111010_2 [4 points]
- 2.4 Simplify the following Boolean expression :

$$\overline{(\overline{ABC})} + \overline{(\overline{ABC})}$$

[3 points]

- 2.5 For the given expression simplify to its sum of products (SOP) form,, Draw the logic circuit for the simplified SOP function.

$$Y = (A+B)(A+\overline{AB})C + \overline{A}(B+\overline{C}) + \overline{AB} + ABC$$

[5 points]

Question 3

Given the logic function $F = \Sigma (0,1,2,3,10,12,13,15)$:

- 3.1 Show the truth table of the function; [5 points]
- 3.2 Obtain an expression for the function F in a sum of products form. [5 points]
- 3.3 Minimize the expression from 3.2 using Boolean algebra theorems. [5 points]
- 4.4 Prove the following Boolean identities using the laws of Boolean algebra:
- (i) $(A + B)(A + C) = A + BC$ [2 points]
- (ii) $ABC + ABC + ABC = A(B + C)$ [3 points]

Question 4

- 4.1 What is a flip-flop? Write the truth table for the clocked J-K flip flop that is triggered by the positive going edge of the clock speed. Explain the operation of this flip flop for the following conditions :Initially all inputs are at zero and assume the Q output to be 1. [10 points]
- 4.2 With the help of a suitable diagram explain how you convert a JK flip flop to a T type flip flop [5 points]
- 4.3 With the help of a suitable diagram explain how do you convert a JK flip flop to a T type flip flop [5 points]

Question 5

- 5.1 Define the term Demultiplexer [2 points]
- 5.2 Explain and design a 1 to 4 Demultiplexer [8 points]
- 5.3 What is a full adder? Explain a full adder with the help of a truth table and logic diagram [10 points]