



**NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY**

**FACULTY OF ENGINEERING**

**DEPARTMENT OF ELECTRONIC ENGINEERING**

**ANALOGUE ELECTRONICS 1**

**EEE2115**

**Examination Paper**

**December 2024**

This examination paper consists of 6 pages

**Time Allowed: 3 hours**

**Total Marks: 100**

**Special Requirements: h - parameter equations and tables**

**Examiner's Name: Mr J. Katekwe**

**INSTRUCTIONS**

- 1 Answer **ALL** questions
- 2 Each question carries 25 marks
- 3 Use of calculators is permissible.

**MARK ALLOCATION**

<b>QUESTION</b>	<b>MARKS</b>
1.	25
2.	25
3.	25
4.	25
<b>Total</b>	<b>100</b>

### QUESTION 1

The transistor parameters for the amplifier shown in Figure 1 are  $h_{fe} = 50$ ,  $h_{ie} = 1.1k\Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$  and  $h_{oe} = 25\mu A$ .

- a. Draw the h-parameter equivalent circuit [4 marks]
- b. Determine:
  - i. The total input impedance [5 marks]
  - ii. The total output impedance [4 marks]
  - iii. Current gain [3 marks]
  - iv. Voltage gain [4 marks]
  - v. Output voltage  $V_o$  peak-peak if  $R_s = 220$  ohms and  $V_i = 30$  millivolts. [5 marks]

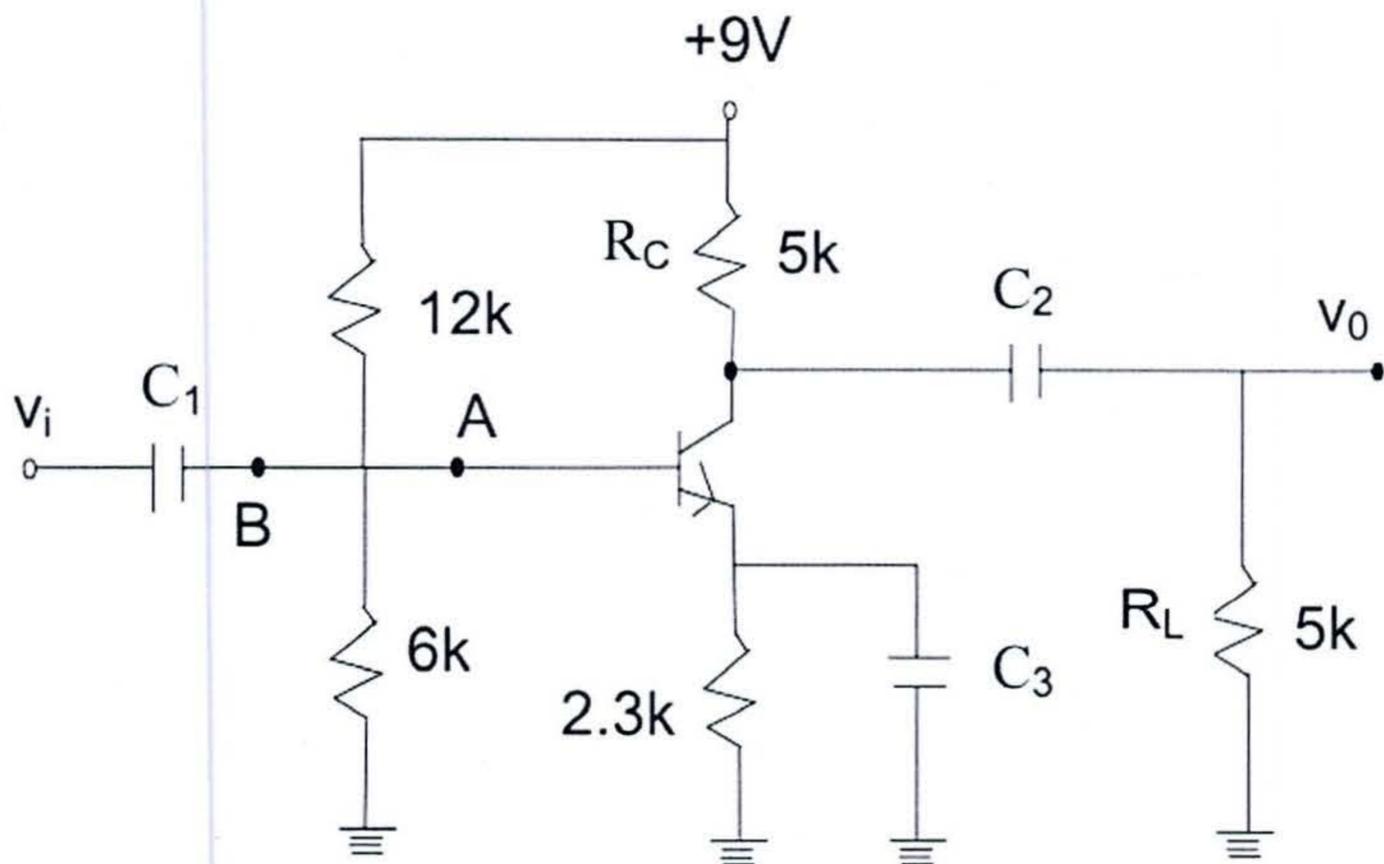


Figure 1

[25 marks]

### QUESTION 2

Figure 2 shows an amplifier with Darlington connected identical transistors Q1 and Q2. The transistors have identical parameters  $h_{fe} = 50$ ,  $h_{ie} = 1.1k\Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$  and  $h_{oe} = 25\mu A$ .

- a. Draw the h-parameter equivalent circuit. [5 marks]
- b. Determine:
  - i. The total input impedance. [7 marks]
  - ii. The total output impedance. [5 marks]
  - iii. Values of the input and output coupling capacitors  $C_1$  and  $C_2$  if the amplifier has a lower cut off frequency of 20Hz. [4 marks]

- iv. Explain the reduction in gain at very low and very high frequencies [4 marks]

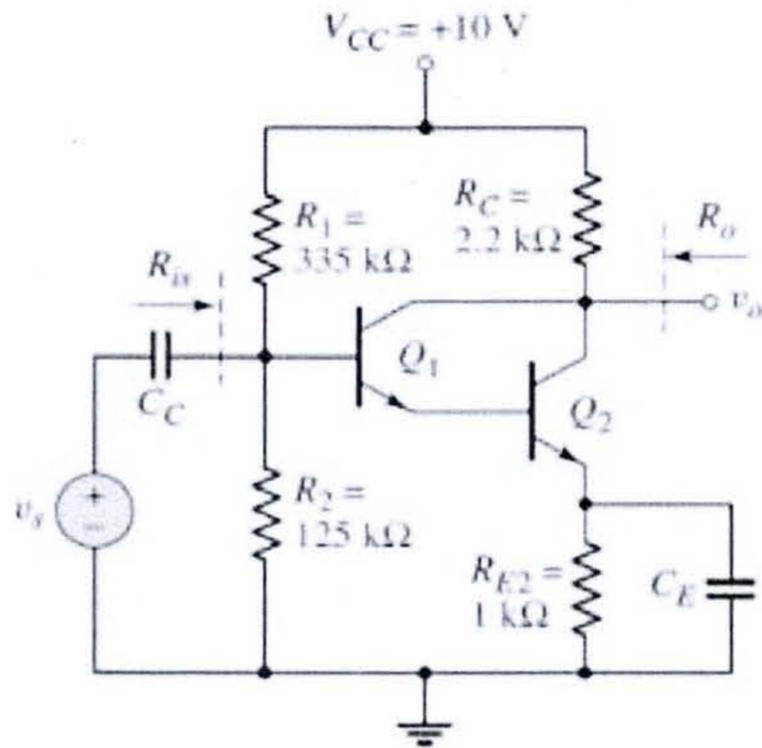


Figure 2

[25 marks]

### QUESTION 3

A differential or long tailed amplifier can be operated in four modes.

- List the four modes of operation of the differential amplifier and draw the schematic diagram for each mode of operation. [4 marks]
- State the 3 properties of differential amplifiers. [3 marks]

The differential amplifier's tail resistor can be replaced with a current source to improve its performance. Figure 3 shows one such current source.

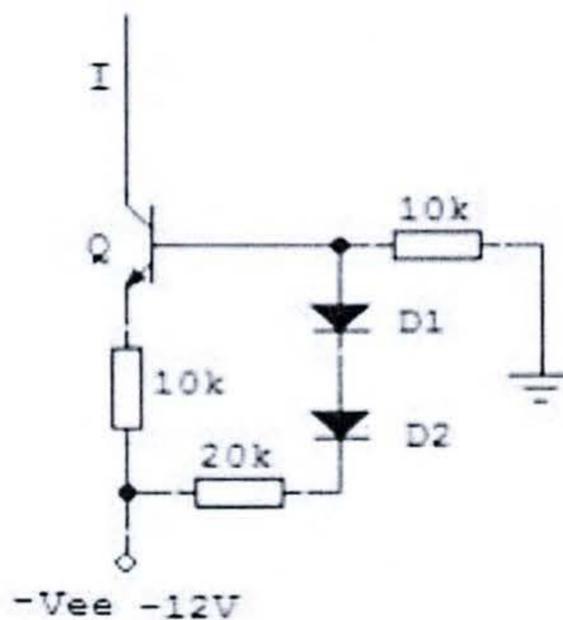


Figure 3

- c. Assuming that the differential amplifier has identical transistors, find the biasing collector current that the current source will supply to each of the two amplifier transistors.

[6 marks]

- d. A negative feedback connected amplifier has a gain of  $13\frac{1}{3}$  and a feedback network gain to open loop gain ratio of  $\frac{1}{3920}$ . Show that the gain of the same amplifier without feedback lies between 200 and 300.

[8 marks]

- e. With the aid of an appropriate waveform, explain the operation of an ideal Class A large signal amplifier with resistive load.

[4 marks]

[25 marks]

#### QUESTION 4

Figure 4 shows a two stage small signal amplifier. The transistor parameters for the two transistors are  $hfe = 50$ ,  $hie = 1.1k\Omega$ ,  $hre = 2.5 \times 10^{-4}$  and  $hoe = 25\mu A$ .

- a. Draw the h-parameter equivalent circuit. [4 marks]

- b. Determine:

i. The total input impedance. [7 marks]

ii. The total output impedance. [3 marks]

iii. The voltage gain. [3 marks]

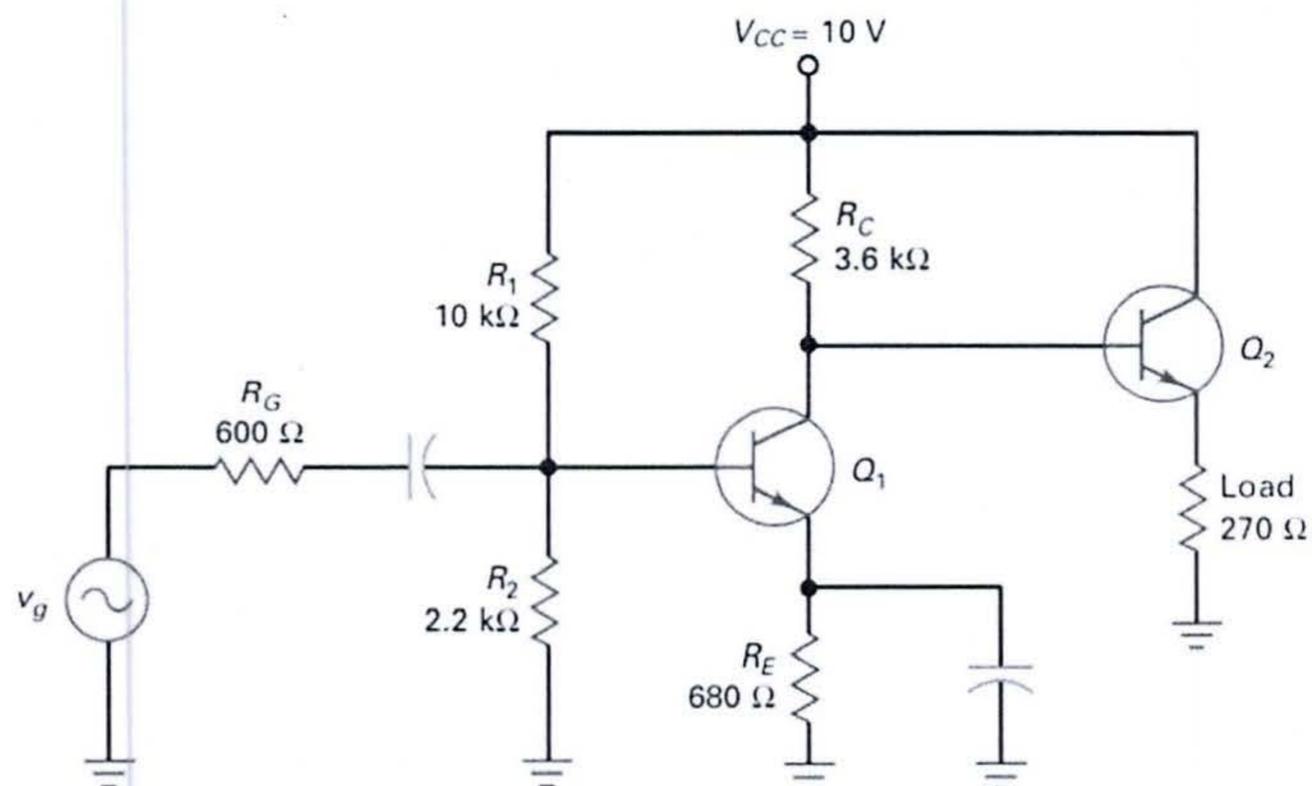


Figure 4

- c. Briefly describe the RC method used for coupling multistage amplifiers with its frequency response. [5 marks]

- d. Compare the RC, Transformer and Direct Coupling methods used in multistage amplifiers in terms of cost, frequency and use. *Tabulate your answer* [3 marks]

[25 marks]



## h-PARAMETER EQUATIONS AND CONVERSION TABLES



Table 1: Generic small signals device h-parameter performance equations	
$Z_i$	$h_{11} - \frac{h_{12}h_{21}}{h_{22} + \frac{1}{R_L}}$
$A_i$	$\frac{h_{21}}{1 + h_{22}R_L}$
$A_v$	$\frac{-h_{21}}{Z_i \left( h_{22} + \frac{1}{R_L} \right)}$
$Z_o$	$\frac{1}{h_{22} - \frac{h_{12}h_{21}}{h_{11}}}$

Table 2: Common emitter to common collector h-parameter conversion	
$h_{ic}$	$h_{ie}$
$h_{fc}$	$-(1 + h_{fe})$
$h_{rc}$	$1 - h_{re}$
$h_{oc}$	$h_{oe}$

Table 3: Common emitter to common base h-parameter conversion	
$h_{ib}$	$\frac{h_{ie}}{h_{oe}h_{ie} + (1 + h_{fe})(1 - h_{re})}$
$h_{fb}$	$\frac{-h_{fe}(1 - h_{re}) - h_{oe}h_{ie}}{h_{oe}h_{ie} + (1 + h_{fe})(1 - h_{re})}$
$h_{rb}$	$\frac{h_{oe}h_{ie} - h_{re}(1 + h_{fe})}{h_{oe}h_{ie} + (1 + h_{fe})(1 - h_{re})}$
$h_{ob}$	$\frac{h_{oe}}{h_{oe}h_{ie} + (1 + h_{fe})(1 - h_{re})}$

Table 4: Darlington pair common emitter h-parameter equations	
$h'_{ie}$	$h_{ie1} + h_{fe1}h_{ie2}$
$h'_{fe}$	$h_{fe1}h_{fe2}$
$h'_{re}$	$\frac{h_{oe1}h_{ie2}}{1 + h_{oe1}h_{ie2}}$
$h'_{oe}$	$\frac{h_{oe1}h_{fe2}}{1 + h_{oe1}h_{ie2}} + h_{oe2}$