



**NATIONAL UNIVERSITY OF SCIENCE AND TECHNOLOGY**

**FACULTY OF ENGINEERING**

**DEPARTMENT OF ELECTRONIC ENGINEERING**

**TEE 2292 Electrical Engineering Principles**

**Supplementary examinations**

**May 2024**

**This examination paper consists of 4 pages**

**Time Allowed: 3 Hours**

**Total Marks: 100**

**Examiner's Name: Eng. J.T. Mwanza**

**INSTRUCTION AND INFORMATION TO THE CANDIDATE**

- 1. Answer ALL parts of Section A and any THREE questions from Section B.**
- 2. Section A carries 40 marks and Section B carries 60 marks.**
- 3. Start each question on a new page**
- 4. Use of calculators is permissible**


**MARK ALLOCATION**

<b><u>QUESTION</u></b>	<b><u>MARKS</u></b>
<b><u>1</u></b>	<b><u>40</u></b>
<b><u>2</u></b>	<b><u>20</u></b>
<b><u>3</u></b>	<b><u>20</u></b>
<b><u>4</u></b>	<b><u>20</u></b>
<b><u>5</u></b>	<b><u>20</u></b>
<b><u>Total marks attainable by candidate</u></b>	<b><u>100</u></b>

SECTION A

Question 1

- a) In the circuit below calculate the current in each of the resistors. If the values are given as follows:  $R_1 = 10\Omega$ ,  $R_2 = 20\Omega$ ,  $R_3 = 30\Omega$ ,  $V_1 = 15\text{ V}$ ,  $V_2 = 20\text{ V}$ . [20 Marks]

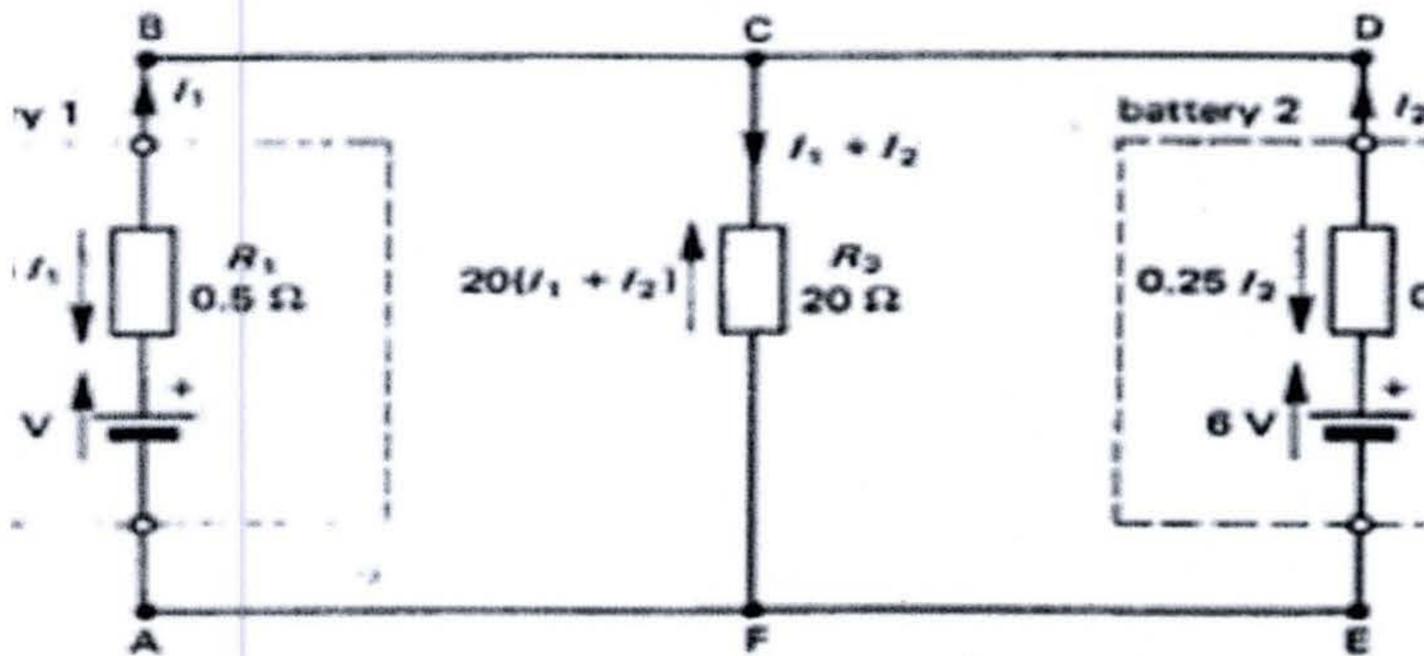

Question 2

- a) With the aid of a diagram, explain the operation of one form of a single-phase AC motor. [10 Marks]
- b) Three resistors of  $10\Omega$ ,  $20\Omega$  and  $10\Omega$  are connected
- In series
  - in parallel

The power consumed in an AC circuit containing a pure resistance is  $200\text{ W}$ . If the supply voltage is  $240\text{ V}$ , determine the current and resistance of the circuit.

[10 Marks]

## SECTION B

### Question 3

- a) Under what circumstances are the following used: a three-phase 4-wire system and a three-phase 3-wire system. **[4 Marks]**
- b) Explain the principle and operation of an induction motor and a synchronous motor in detail by drawing suitable diagrams. **[16 Marks]**

### Question 4

- a) Explain the terms:
- self-induction,
  - induction by motion,
  - mutual induction.
- [12 Marks]**
- b) An inductor has an inductive reactance of  $10\Omega$  at a frequency of 100Hz. Calculate the reactance of the inductor at a frequency of
- 50 Hz
  - 400 Hz
  - 1 500 Hz

If the supply voltage is 100 V rms, determine the current in the inductor for each frequency. **[8 Marks]**

### Question 5

- a) What is meant by: inductive reactance and capacitive reactance? Circuit A contains an inductance of reactance  $150\Omega$  and circuit B contains a capacitance of reactance  $80\Omega$ . If the supply voltage is 100V, calculate for each circuit the current in the circuit and the phase angle of the circuit. **[10 Marks]**
- b) Draw 4 types of DC machines and give some applications for each of them. **[8 Marks]**
- c) Calculate the mean value of a sinusoidal voltage wave whose maximum value is 100 V. Determine also the maximum value of a voltage wave whose average value is 90V. **[2 Marks]**

### Question 6

- a) Calculate the speed of the rotating field of a 2-pole motor in rev/min if the supply frequency is: 50Hz and 60Hz. What is the synchronous speed if the motor has 2 pole-pairs ( two N poles and two S poles). **[8 Marks]**
- b) Define the following active voltage, active current, reactive voltage, reactive current **[8 Marks]**
- c) A 50Hz, four-pole induction motor has a fractional slip of 5%. Calculate the speed of the motor. **[4 Marks]**